

- Aim : To verify Kirchhoff's Current Law & Kirchhoff's Voltage Law.
- Apparatus : DC power supply, Ammeter, voltmeter (0-150V),  
Rheostat, multimeter.
- Theory :

KCL states, the algebraic sum of all currents entering and exiting a node must be equal to zero  
i.e.  $\sum_{i=1}^n I_i = 0$  - Eqn 1

$I_i$  - current entering from branch  $i$  to a node  
Total  $n$  branches.

KVL states that the directed sum of the potential difference around any closed loop is zero.

i.e.  $\sum_{k=1}^n V_k$  - Eqn 2

$n$  - total no. of voltage drop measured.

- Procedure :



A. To verify Kirchhoff's Law -

1. Connect the circuit as shown in Fig. I

2. Set the values of rheostat to  $R_1 = 145\Omega$  and  $R_2 = 300\Omega$  and  $R_3 = 145\Omega$

3. Connect ammeter in series with each resistor.

## Circuit Diagram

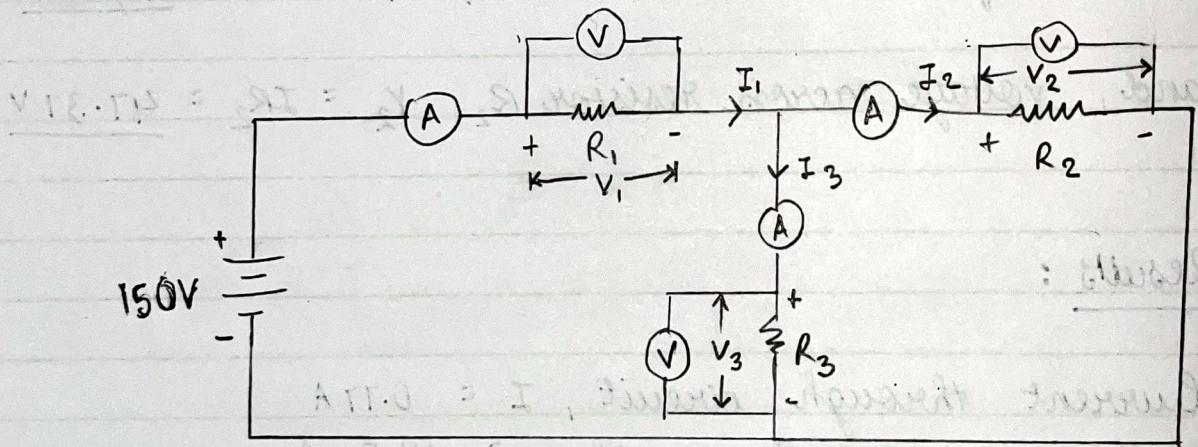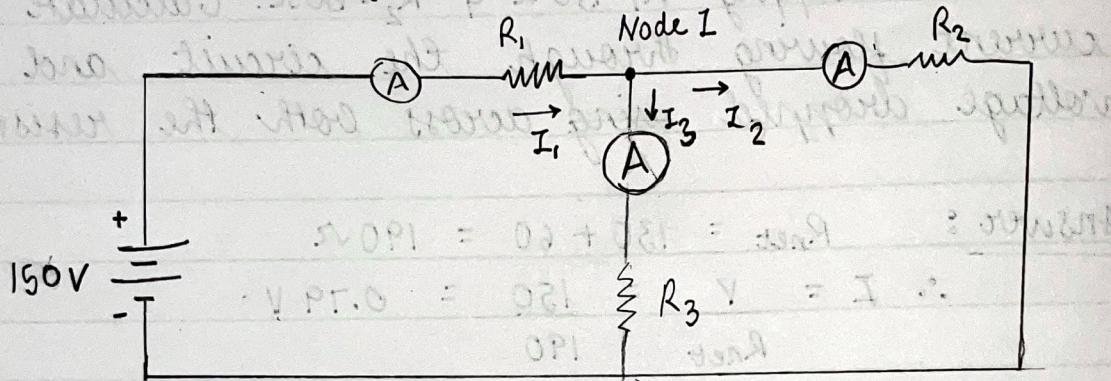

(v) trifft unter betrachteter Quelle somit auf  
trifft unter betrachteter Quelle somit auf  
trifft unter betrachteter Quelle somit auf  
trifft unter betrachteter Quelle somit auf

- 4- Turn ON the DC power supply, measure the supply given to circuit using multimeter and set its value to 156V.
- 5- Observe the current shown in each ammeter and note it down.
- 6- Using Eqn 1 verify Kirchhoff's law.

B To verify Kirchhoff's Voltage Law :

- 1- Connect the circuit as shown in Fig-2
- 2- Set the values of rheostat to  $R_1 = 145\Omega$ ,  $R_2 = 300\Omega$  and  $R_3 = 145\Omega$ .
- 3- Connect voltmeter in parallel with each resistor.
- 4- Turn ON the DC supply, measure the supply given to circuit using Multimeter and set its value to 156 V.
- 5- Observe the current shown in each voltmeter and note it down.
- 6- Using Eqn 2 verify Kirchhoff's Voltage Law.

• Questions :

- 1) For a resistive circuit as shown in Fig.1 with 150V DC supply,  $R_1 = 100\Omega$  and  $R_2 = 200\Omega$  and  $R_3 = 150\Omega$ . Calculate the current flowing through each resistor and verify KCL at Node L.
- 2) For a resistive circuit as shown in Fig.2

# Circuits

## Observation Table :

$$R_1 = 145\Omega \quad R_2 = 300\Omega \\ R_3 = 145\Omega \quad V = 156V$$

Current through Resistors	Observed Values	Calculated Values
$I_1$	0.65 A	0.64 A
$I_2$	0.21 A	0.21 A
$I_3$	0.45 A	0.43 A

Voltage across Resistors	Observed Values	Calculated Values
$V_1$	93 V	92.8 V
$V_2$	62 V	63 V
$V_3$	62 V	63 V

## Calculations :

[Observed values] Verification

$$\rightarrow 0.21 + 0.45 = 0.66 \approx 0.65$$

[KCL]

$$\text{From KCL} \rightarrow 93 + 62 = 155 \approx 156V$$

$$I_1 = I_2 + I_3$$

$$I_1 = \frac{V}{R_1 + R_2 R_3 / R_2 + R_3} = 0.64 A$$

$$I_2 = \frac{145 \times 0.64}{300} = 0.21 A$$

$$\therefore I_3 = \frac{300 \times 0.64}{145} = 0.43 A$$

$$\text{From KVL, } V_1 + V_2 = 156V$$

$$V_1 = I_1 R_1 = 92.8 V$$

$$V_2 = I_2 R_2 = 63 V$$

$$V_3 = I_3 R_3 = 63 V$$

## Calculations Q1 -

$$R_1 = 100\Omega, R_2 = 200\Omega, R_3 = 150\Omega, V = 150V$$

$$R_{\text{net}} = 100 + \frac{(200)(150)}{350} = \underline{\underline{185.71\Omega}}$$

$$\therefore I_1 = \frac{150}{185.71} = \underline{\underline{0.81A}}$$

$$\therefore I_2 = \frac{3}{7}(0.81) = \underline{\underline{0.35A}}$$

$$I_3 = \frac{4}{7}(0.81) = \underline{\underline{0.46A}}$$

$\therefore$  At Node I

$$I_1 = 0.81 \Rightarrow I_2 + I_3 = \underline{\underline{0.81A}}$$

KCL verified

## Calculation Q2 -

$$R_1 = 100\Omega, R_2 = 200\Omega, R_3 = 150\Omega, V = 150V$$

$$V_1 = I_1 R_1 = 0.81 \times 100 \\ = \underline{\underline{81V}}$$

$$V_2 = I_2 R_2 = \underline{\underline{70V}}$$

$$V_3 = I_3 R_3 = 0.46 \times 150 \\ = \underline{\underline{69V}}$$

$$V = V_1 + V_2 \\ (\underline{\underline{V_2 \approx V_3}})$$

with 150V DC supply,  $R_1 = 100\Omega$ ,  $R_2 = 200\Omega$  &  $R_3 = 150\Omega$ . Calculate the voltage across each resistor and verify KVL.

- Results :

A.1  $I_1 = 0.81A$ ,  $I_2 = 0.35A$ ,  $I_3 = 0.46A$   
 $\therefore$  In KCL LHS = RHS  $\therefore$  Verified

A.2  $I_1 = V_1 = 81V$ ,  $V_2 = 70V$ ,  $V_3 = 69V$  [Ignoring calc. approximations]  
 $\therefore$  In KCL LHS = RHS Verified

- Conclusions :

1. Kirchhoff's Current & Voltage Laws are verified for an electric circuit.
2. Minor calculations, or instrumental errors are ignored. (approximations)
3. Instrumental errors are possible due resistance of the ammeter & voltmeter & also of the wires.