

Assignment 5

Design circuit for 1 bit ALU that performs SUB, NAND and NOR operations in logisim simulation tool.

Instructions:

Make a zip of the following and upload in the classroom.

- PDF document consisting of circuit image(s).
- Circuit file.