



# Digital Electronics & Logic Design

(EC 207)



**Dr. Vivek Garg**

Department of Electronics Engineering  
S. V. National Institute of Technology (SVNIT)  
Surat

email: [vivekg@eced.svnit.ac.in](mailto:vivekg@eced.svnit.ac.in); [vivekgarg0101@gmail.com](mailto:vivekgarg0101@gmail.com)



# Course Outline



- **PN DIODE AND TRANSITOR (04 Hours)**  
PN Diode Theory, PN Characteristic and Breakdown Region, PN Diode Application as Rectifier, Zener Diode Theory, Zener Voltage Regulator, Diode as Clamper and Clipper, Photodiode Theory, LED Theory, 7 Segment LED Circuit Diagram and Multi Colour LED, LASER Diode Theory and Applications, Bipolar Junction Transistor Theory, Transistor Symbols And Terminals, Common Collector, Emitter and Base Configurations, Different Biasing Techniques, Concept of Transistor Amplifier, Introduction to FET Transistor And Its Feature.
- **WAVESHAPING CIRCUITS AND OPERATIONAL AMPLIFIER (06 Hours)**  
Linear Wave Shaping Circuits, RC High Pass and Low Pass Circuits, RC Integrator and Differentiator Circuits, Nonlinear Wave Shaping Circuits, Two Level Diode Clipper Circuits, Clamping Circuits, Operational Amplifier OP-AMP with Block Diagram, Schematic Symbol of OP-AMP, The 741 Package Style and Pinouts, Specifications of Op-Amp, Inverting and Non-Inverting Amplifier, Voltage Follower Circuit, Multistage OP-AMP Circuit, OP-AMP Averaging Amplifier, OP-AMP Subtractor.
- **BOOLEAN ALGEBRA AND SWITCHING FUNCTIONS (04 Hours)**  
Basic Logic Operation and Logic Gates, Truth Table, Basic Postulates and Fundamental Theorems of Boolean Algebra, Standard Representations of Logic Functions- SOP and POS Forms, Simplification of Switching Functions-K-Map and Quine-Mccluskey Tabular Methods, Synthesis of Combinational Logic Circuits.
- **COMBINATIONAL LOGIC CIRCUIT USING MSI INTEGRATED CIRCUITS (07 Hours)**



# Course Outline



Binary Parallel Adder; BCD Adder; Encoder, Priority Encoder, Decoder; Multiplexer and Demultiplexer Circuits; Implementation of Boolean Functions Using Decoder and Multiplexer; Arithmetic and Logic Unit; BCD to 7-Segment Decoder; Common Anode and Common Cathode 7-Segment Displays; Random Access Memory, Read Only Memory And Erasable Programmable ROMS; Programmable Logic Array (PLA) and Programmable Array Logic (PAL).

- **INTRODUCTION TO SEQUENTIAL LOGIC CIRCUITS** **(04 Hours)**  
Basic Concepts of Sequential Circuits; Cross Coupled SR Flip-Flop Using NAND or NOR Gates; JK Flip-Flop Rise Condition; Clocked Flip-Flop; D-Type and Toggle Flip-Flops; Truth Tables and Excitation Tables for Flip-Flops; Master Slave Configuration; Edge Triggered and Level Triggered Flip-Flops; Elimination of Switch Bounce using Flip-Flops; Flip-Flops with Preset and Clear.
- **SEQUENTIAL LOGIC CIRCUIT DESIGN** **(06 Hours)**  
Basic Concepts of Counters and Registers; Binary Counters; BCD Counters; Up Down Counter; Johnson Counter, Module-N Counter; Design of Counter Using State Diagrams and Table; Sequence Generators; Shift Left and Right Register; Registers With Parallel Load; Serial-In-Parallel-Out (SIPO) And Parallel-In-Serial-Out(PISO); Register using Different Type of Flip-Flop.
- **REGISTER TRANSFER LOGIC** **(04 Hours)**  
Arithmetic, Logic and Shift Micro-Operation; Conditional Control Statements; Fixed-Point and Floating-Point Data; Arithmetic Shifts; Instruction Code and Design Of Simple Computer.
- **PROCESSOR LOGIC DESIGN** **(03 Hours)**  
Processor Organization; Design of Arithmetic Logic Unit; Design of Accumulator.
- **CONTROL LOGIC DESIGN** **(04 Hours)**  
Control Organization; Hard-Wired Control; Micro Program Control; Control Of Processor Unit; PLA Control.



# Course Text and Materials



1. Schilling Donald L. and Belove E., "Electronics Circuits- Discrete and Integrated", 3rd Ed., McGraw-Hill, 1989, Reprint 2008.
2. Millman Jacob, Halkias Christos C. and Parikh C., "Integrated Electronics", 2nd Ed., McGraw-Hill, 2009.
3. Taub H. and Mothibi Suryaprakash, Millman J., "Pulse, Digital and Switching Waveforms", 2nd Ed., McGraw-Hill, 2007.
4. Mano Morris, "Digital Logic and Computer Design", 5th Ed., Pearson Education, 2005.
5. Lee Samuel, "Digital Circuits and Logic Design", 1st Ed., PHI, 1998.



# Digital Logic Circuits



## Shift Registers

- An array of flip flop is used to store a group of bits.
- To store  $n$  bits,  $n$  flip flops are cascaded.
- **Types:** 1. Based on input and outputs

Serial In Serial Out

Serial in Parallel Out

Parallel in Serial Out

Parallel in Parallel Out

### 2. Based on application

Shift Register


Storage Register



# Digital Logic Circuits



## Serial In Serial Out

 

- For n bit storage n clock pulse is required.
- It provides n clock pulse delay
- To get n bit serial out, n-1 clock pulses are required.



# Digital Logic Circuits



## Serial In Serial Out

CLK	FF0 ( $Q_0$ )	FF1 ( $Q_1$ )	FF2 ( $Q_2$ )	FF3 ( $Q_3$ )
Initial	0	0	0	0
1	0	0	0	0
2	1	0	0	0
3	0	1	0	0
4	1	0	1	0

CLK	FF0 ( $Q_0$ )	FF1 ( $Q_1$ )	FF2 ( $Q_2$ )	FF3 ( $Q_3$ )
Initial	1	0	1	0
5	0	1	0	1
6	0	0	1	0
7	0	0	0	1
8	0	0	0	0






# Digital Logic Circuits



## Serial In Serial Out

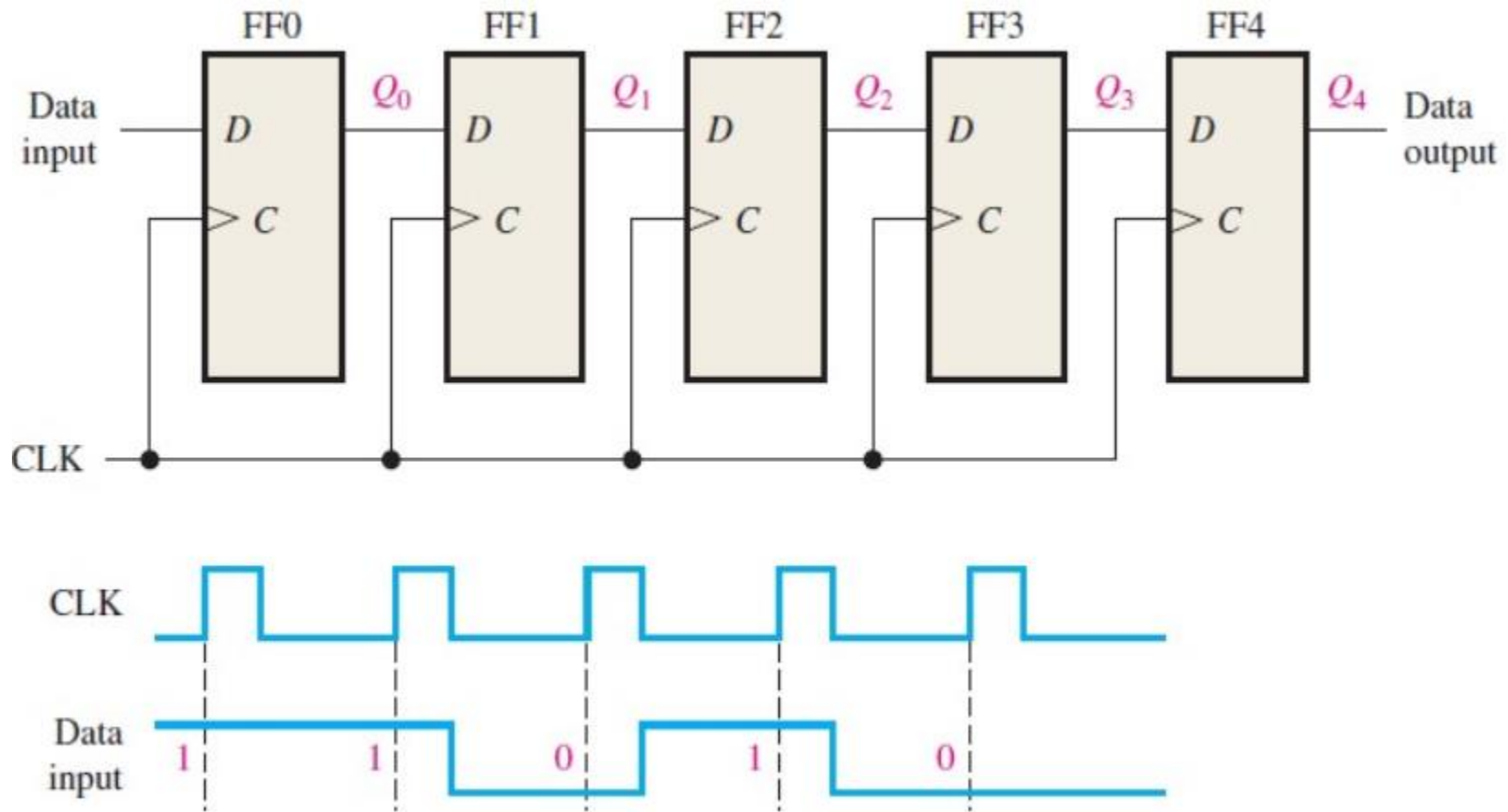






# Digital Logic Circuits



## Serial In Serial Out

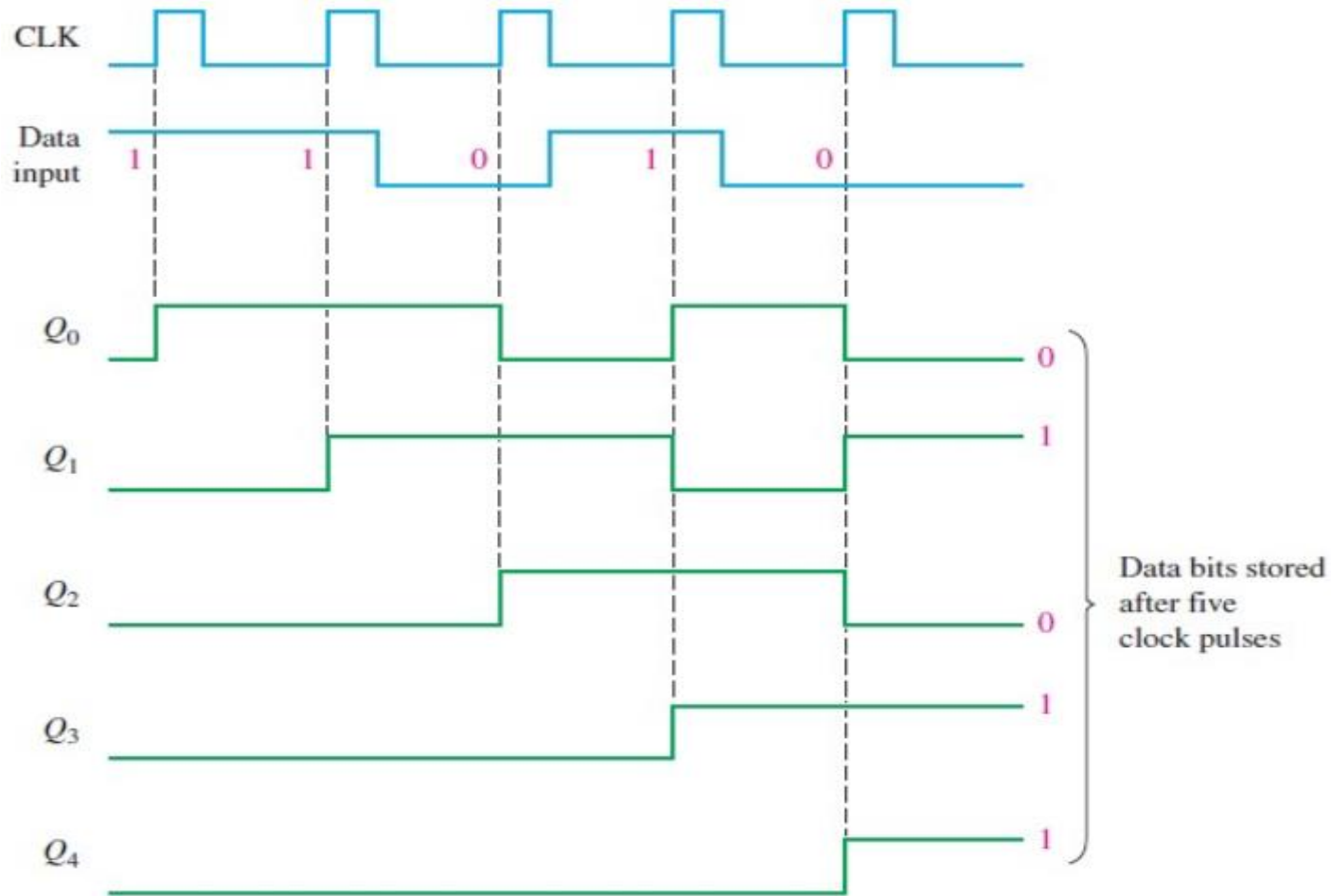





# Digital Logic Circuits



## Serial In Parallel Out

 

 - For n bit storage n clock pulse is required.
- For Parallel output, it requires 0 clock pulses.
- It is used as serial to parallel convertor






# Digital Logic Circuits



## Serial In Parallel Out

 




# Digital Logic Circuits



## Parallel In Serial Out


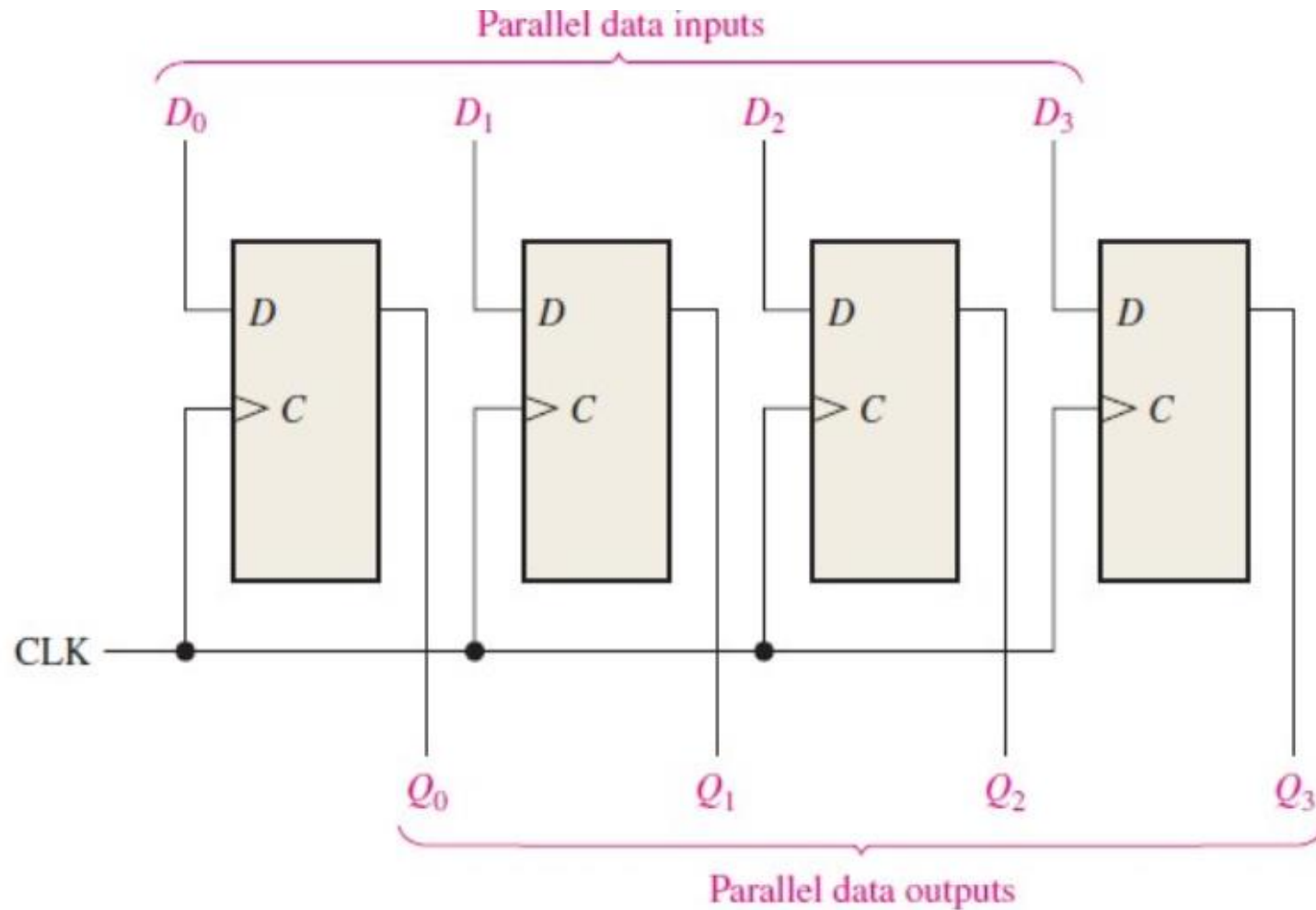




# Digital Logic Circuits



## Parallel In Serial Out

 
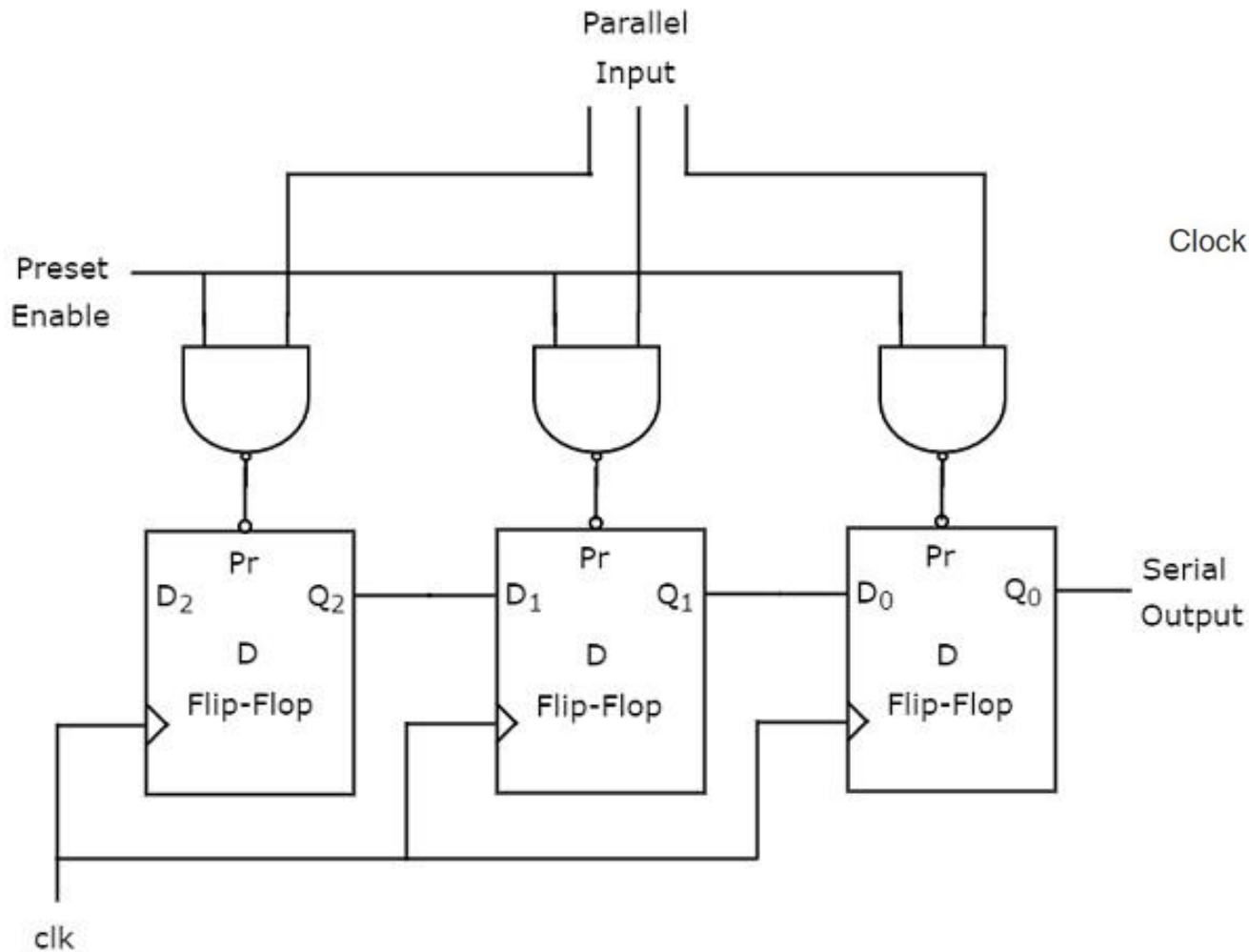




# Digital Logic Circuits



## Parallel In Parallel Out

 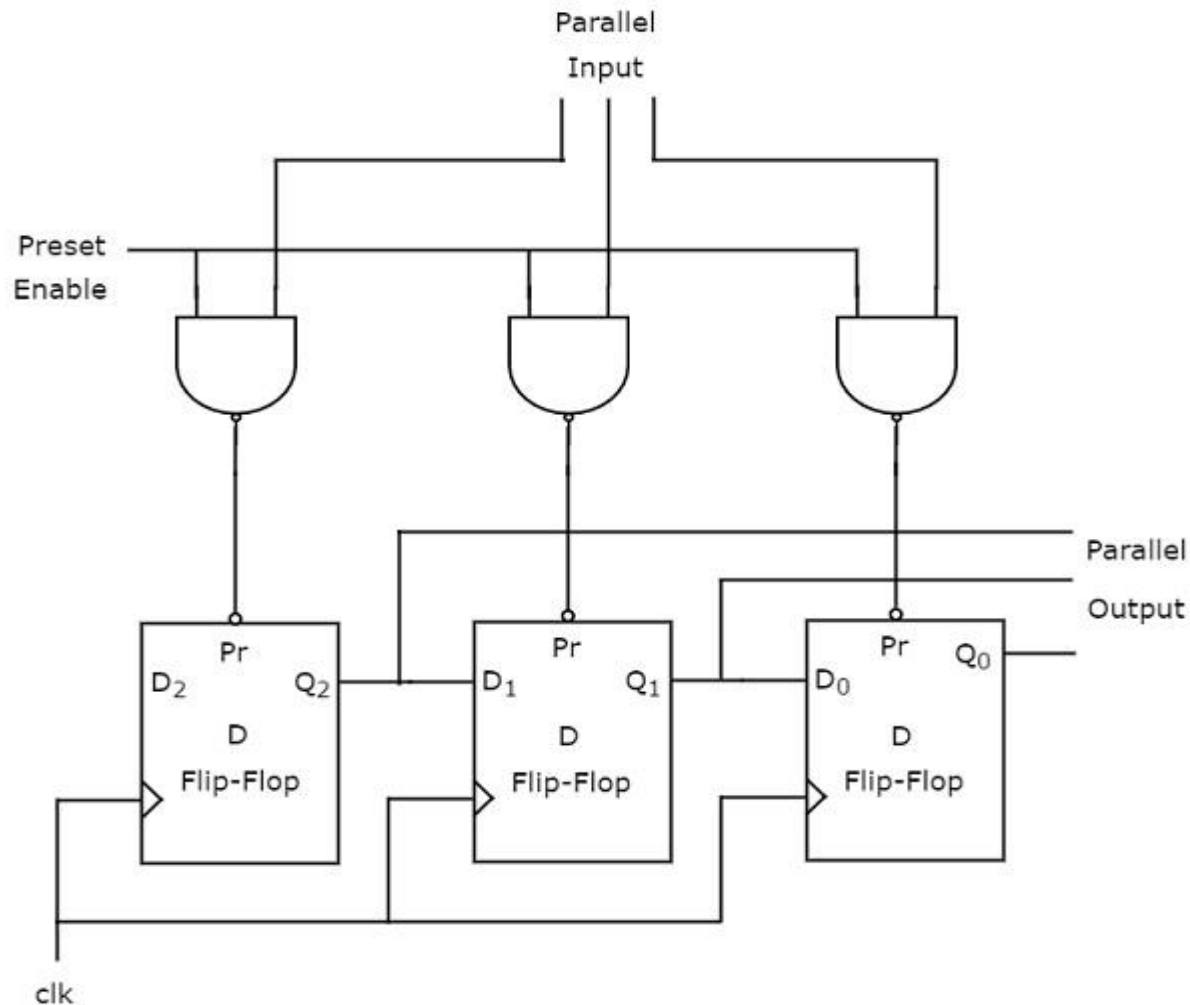




# Digital Logic Circuits


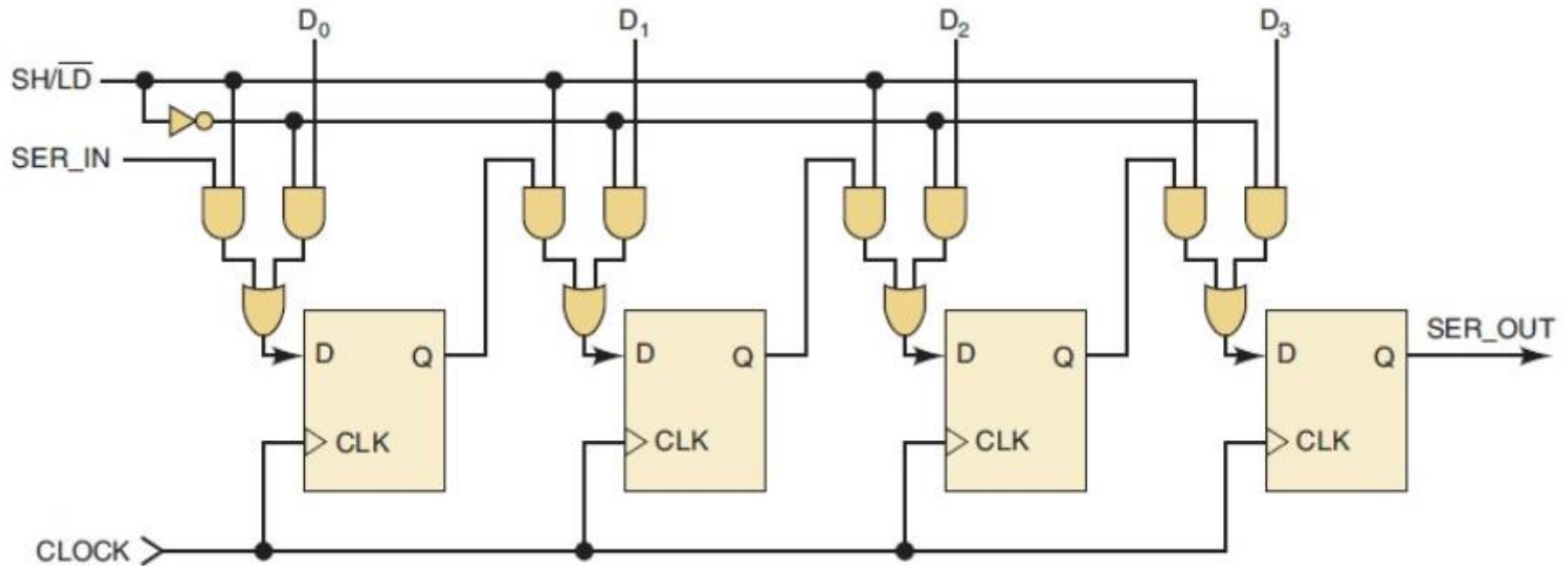
## Parallel/Serial Input and Serial Output








# Digital Logic Circuits



## Bi-Directional Shift Registers

 




# Digital Logic Circuits



## Universal Shift Registers

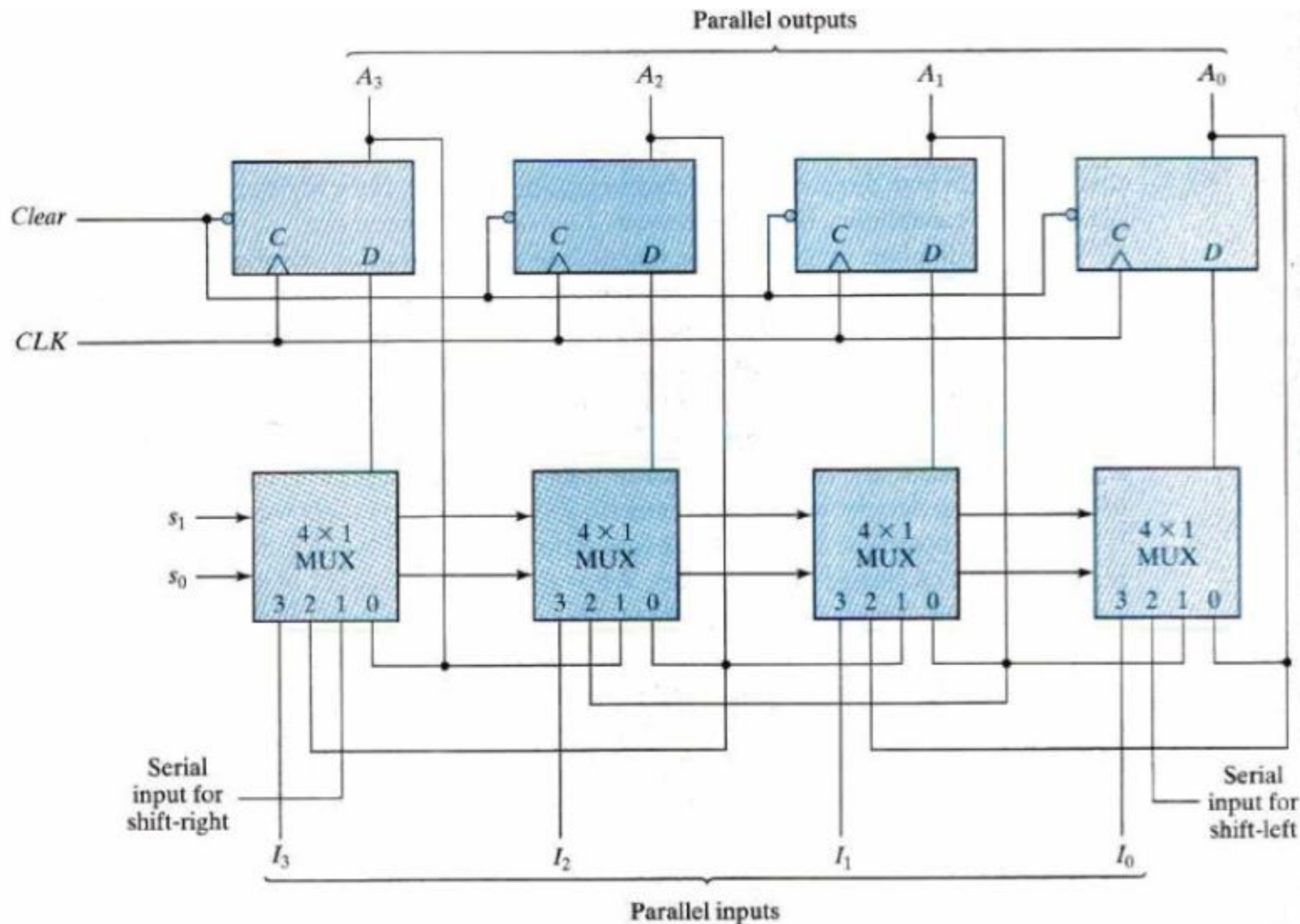


Mode Control		Register Operation
$s_1$	$s_0$	
0	0	No change
0	1	Shift right
1	0	Shift left
1	1	Parallel load



# Digital Logic Circuits



## Shift Registers : Time Delay

 




# Digital Logic Circuits



## Shift Registers : Time Delay

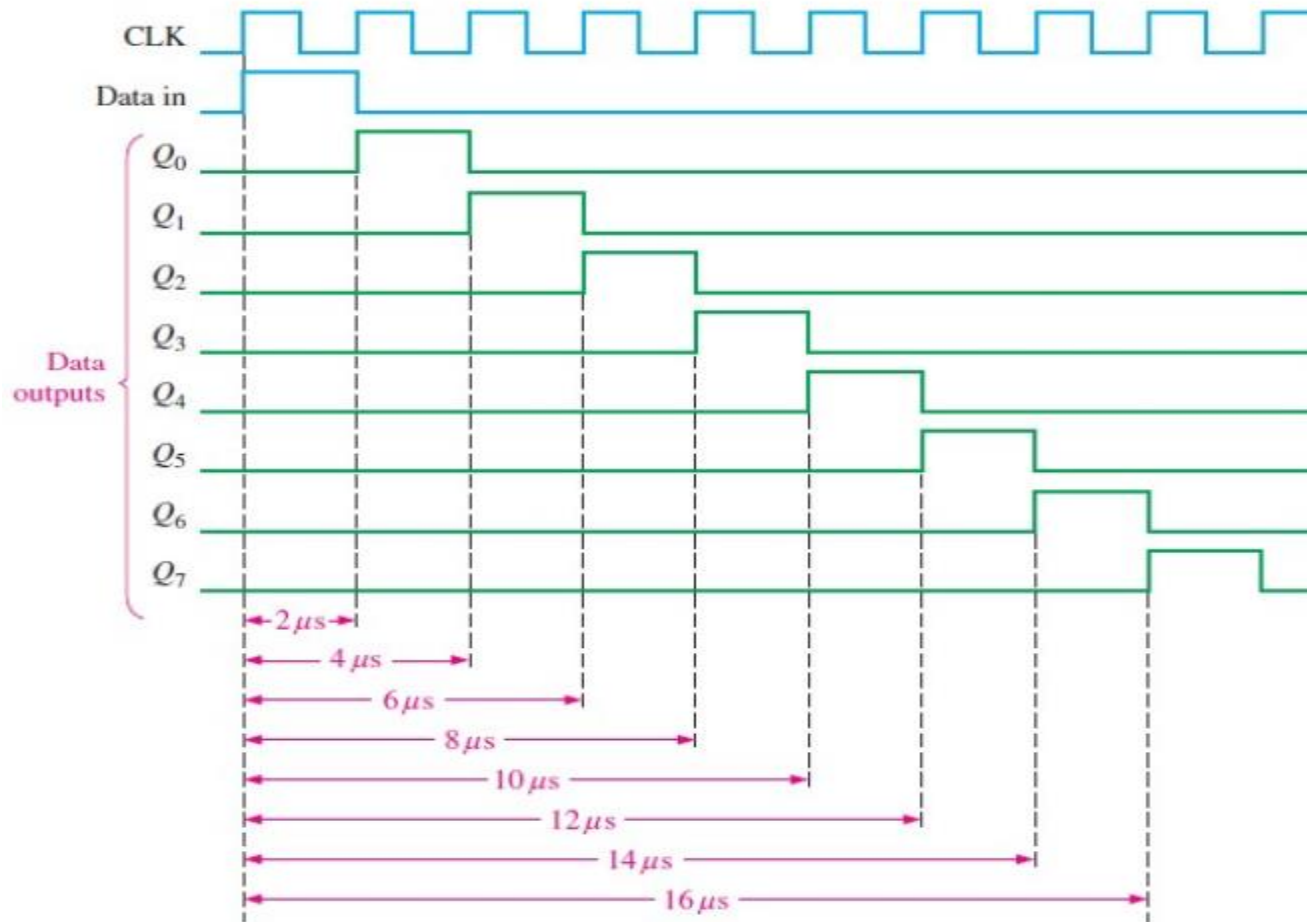



# Digital Logic Circuits



## Counters



- Used to count number of clock pulse is applied.
- Frequency divider
- Time/Frequency measurement
- Pulse Width
- Waveform Generator
- With 'n' FF, maximum possible stages are  $2^n$ .
- **Types of counters:** (Based on the way of clock pulse is applied):
  - a) Asynchronous
  - b) Synchronous



# Digital Logic Circuits



## Asynchronous

 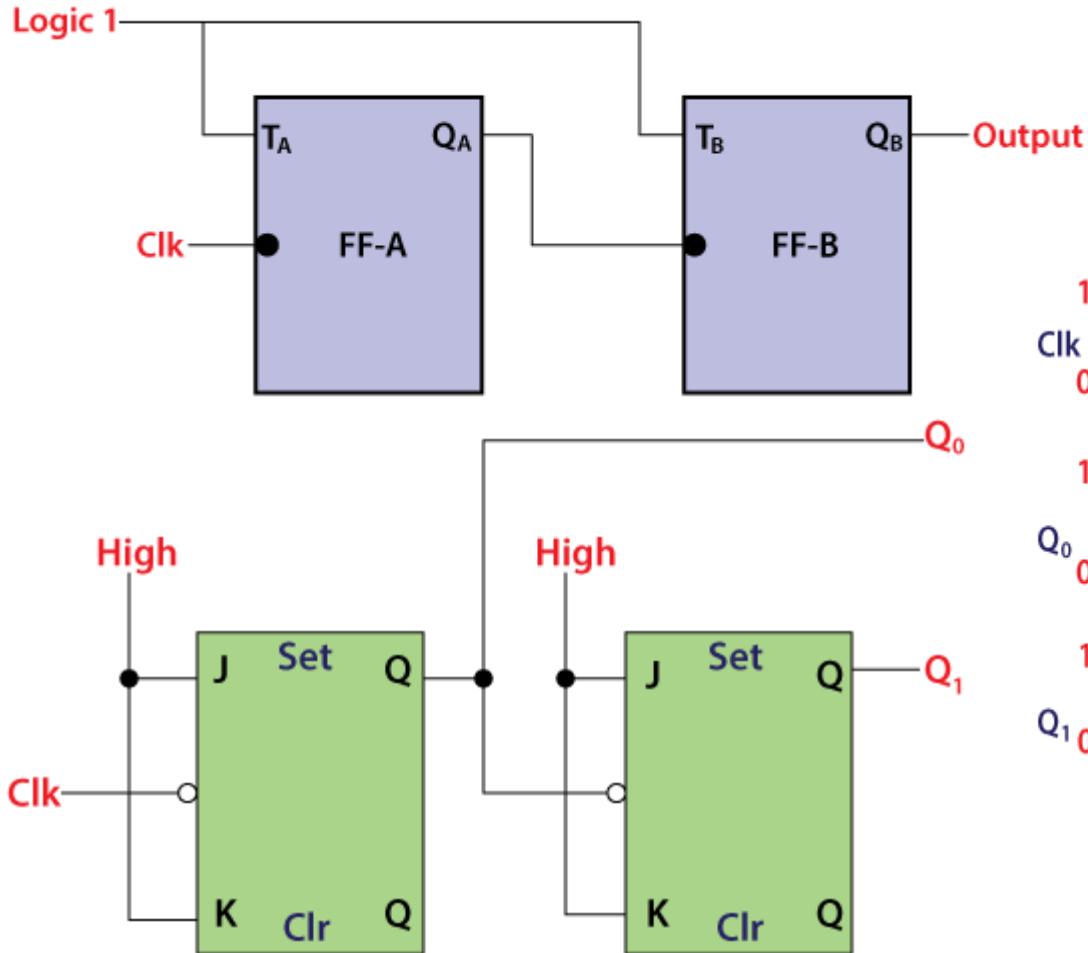




# Digital Logic Circuits



## Synchronous

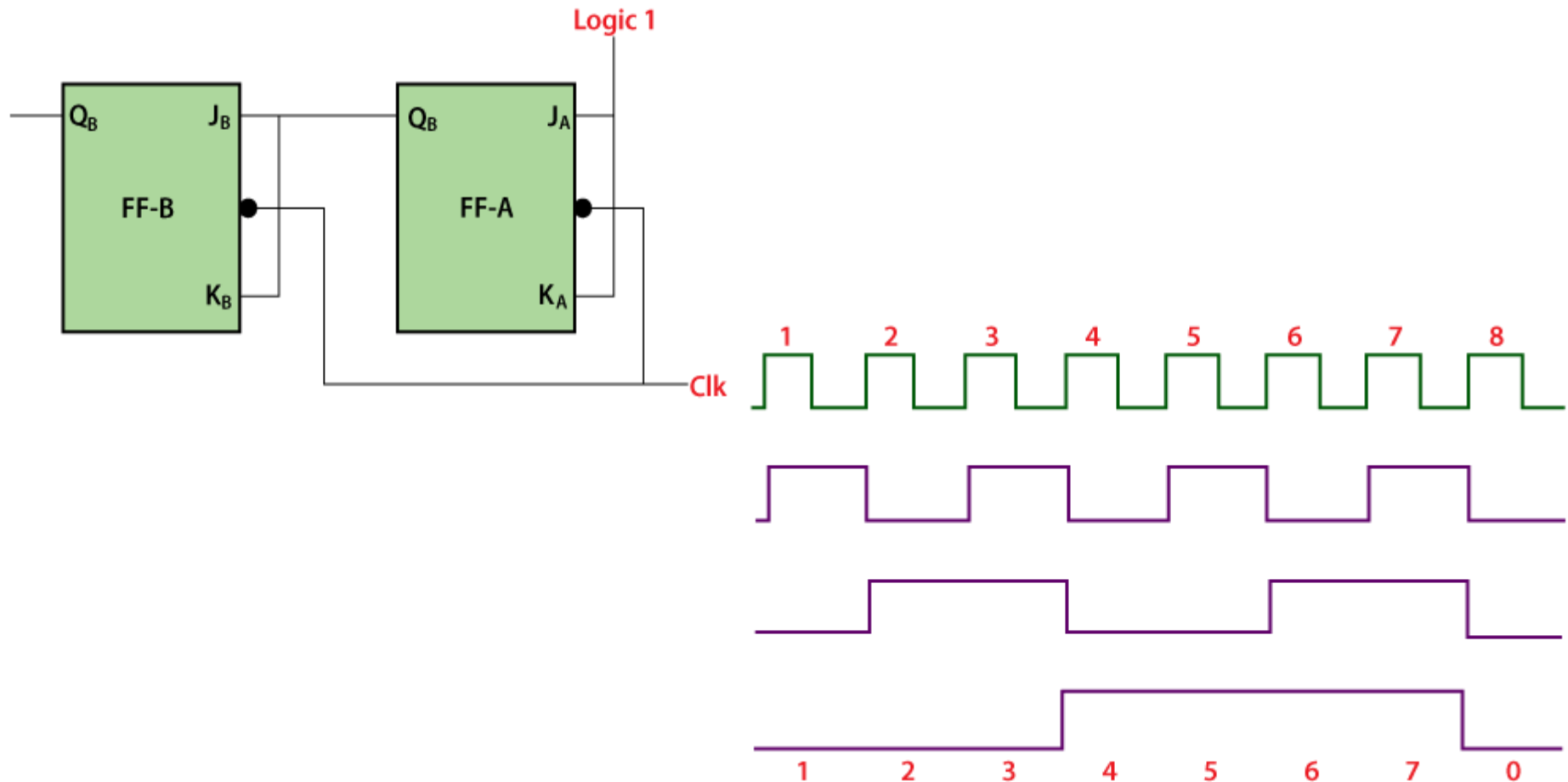





# Digital Logic Circuits



## Ripple/Asynchronous/Serial Counter

- ❑ Cascaded arrangement of Flip-Flops where the output of one Flip-Flop drives the input of the following Flip-Flop.
- ❑ The clock input to any subsequent flip-flop comes from the output of its immediately preceding flip-flop. For instance, the output of the first flip-flop acts as the clock input to the second flip-flop, the output of the second flip-flop feeds the clock input of the third flip-flop and so on.
- ❑ The modulus (MOD number) of a counter is the number of unique states it goes through before it comes back to the initial state to repeat the count sequence.
- ❑ An  $n$ -bit counter that counts through all its natural states and does not skip any of the states has a modulus of  $2^n$ .
- ❑ We can see that such counters have a modulus that is an integral power of 2, that is, 2, 4, 8, 16 and so on.
- ❑ These can be modified with the help of additional combinational logic to get a modulus of less than  $2^n$ .



# Digital Logic Circuits



## Ripple/Asynchronous/Serial Counter

- For given modulus value, number of flip flops required:

$$modulus \leq 2^N$$


- It is desired to design a binary ripple counter that is capable of counting the number of items passing on a conveyor belt. Each time an item passes a given point, a pulse is generated that can be used as a clock input. If the maximum number of items to be counted is 6000, determine the number of flip-flops required.



# Digital Logic Circuits



## Ripple/Asynchronous/Serial Counter

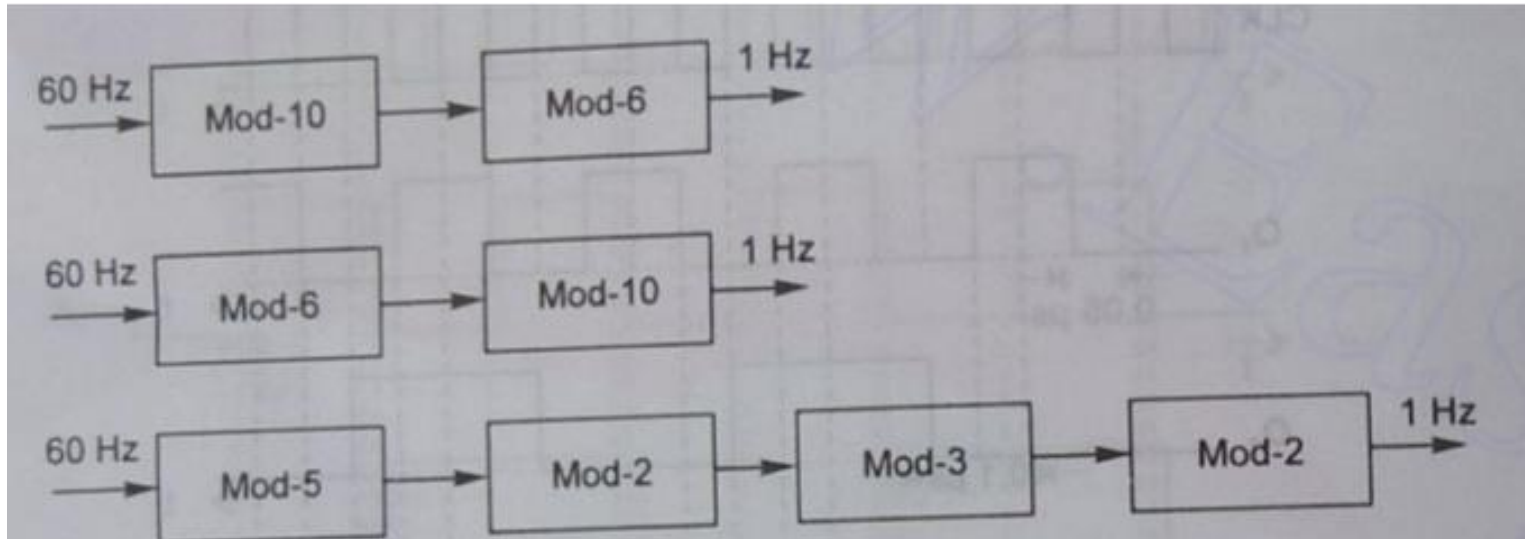




# Digital Logic Circuits




## Ripple/Asynchronous/Serial Counter
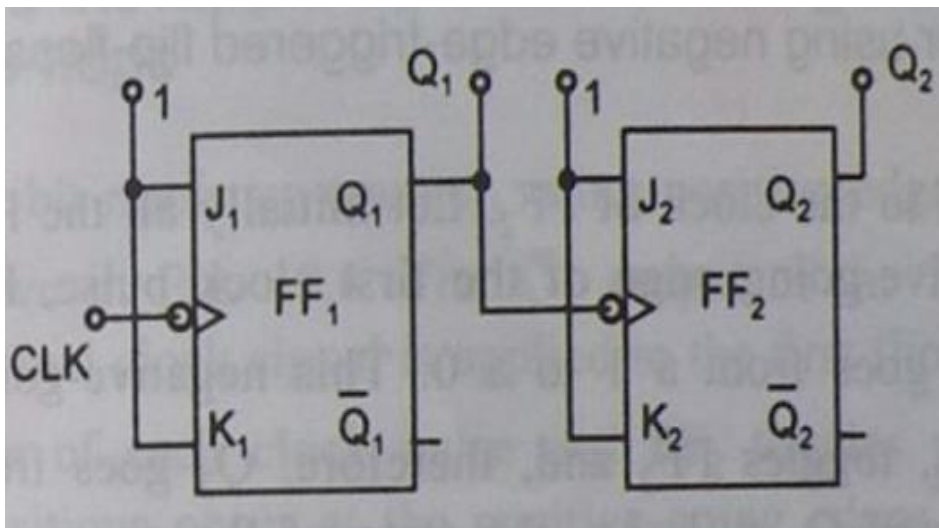
### 2 Bit Negative Edge Triggered UP Counter



Clock Pulse	Q2	Q1
0	0	0
1	0	1
2	1	0
3	1	1
4	0	0

 




# Digital Logic Circuits



## Ripple/Asynchronous/Serial Counter
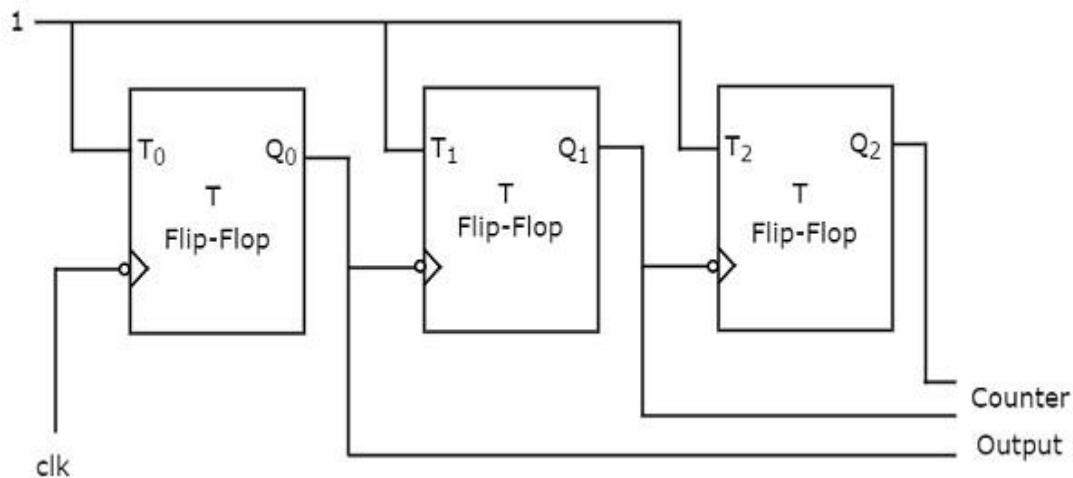
### 3 Bit Negative Edge Triggered UP Counter



Clock Pulse No.	Q3	Q2	Q1
0	0	0	0
1	0	0	1
2	0	1	0
3	0	1	1
4	1	0	0
5	1	0	1
6	1	1	0
7	1	1	1
8	0	0	0




# Digital Logic Circuits




## Ripple/Asynchronous/Serial Counter
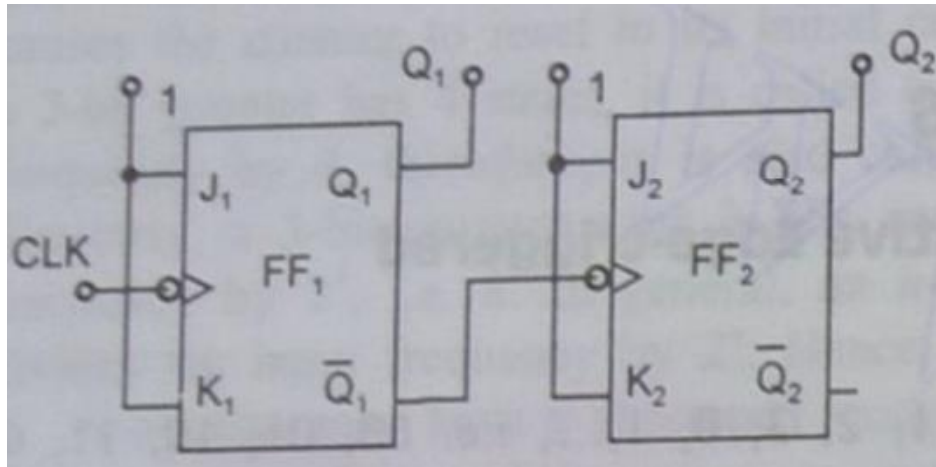
### 2 Bit Negative Edge Triggered Down Counter



Clock Pulse	Q2	Q1	Q1'
0	0	0	1
1	1	1	0
2	1	0	1
3	0	1	0
4	0	0	1

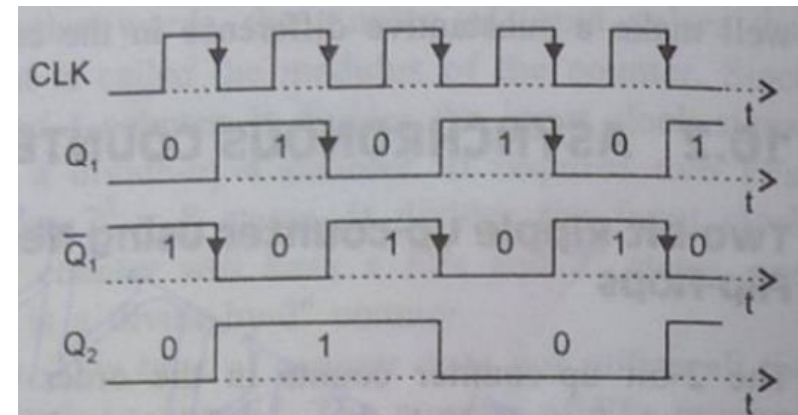



# Digital Logic Circuits



## Ripple/Asynchronous/Serial Counter

### 3 Bit Negative Edge Triggered Down Counter

Clock Pulse No.	Q3	Q2	Q2'	Q1	Q1'
0	0	0	1	0	1
1	1	1	0	1	0
2	1	1	0	0	1
3	1	0	1	1	0
4	1	0	1	0	1
5	0	1	0	1	0
6	0	1	0	0	1
7	0	0	1	1	0
8	0	0	1	0	1






# Digital Logic Circuits


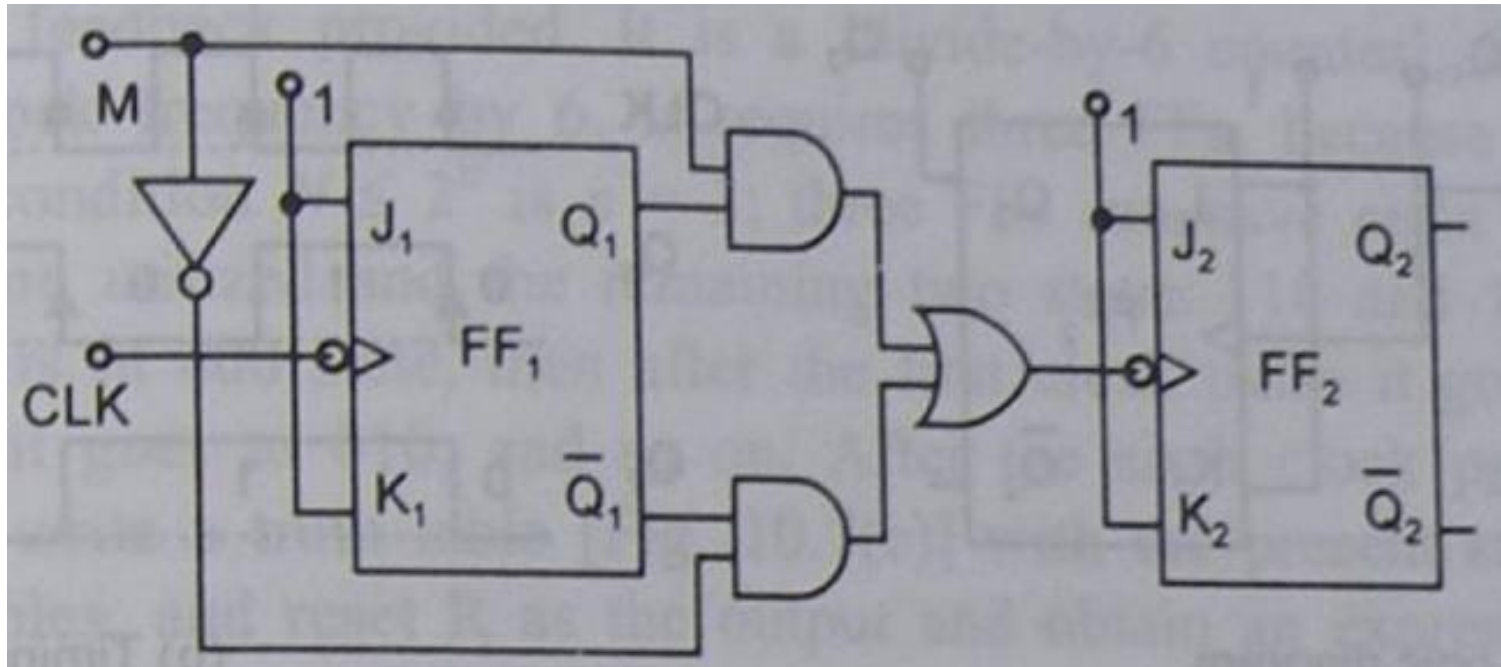
## Ripple/Asynchronous/Serial Counter (UP/Down Counter)






# Digital Logic Circuits




## Ripple/Asynchronous/Serial Counter
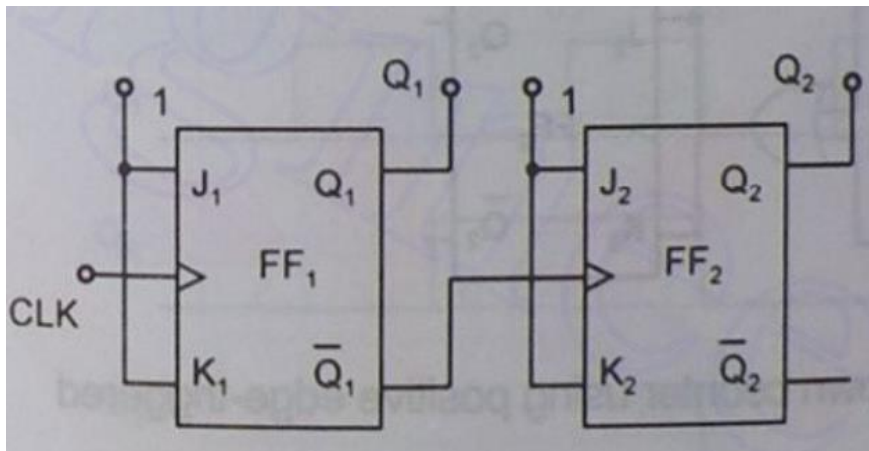
### 2 Bit Positive Edge Triggered Up Counter



Clock Pulse	Q2	Q1	Q1'
0	0	0	1
1	0	1	0
2	1	0	1
3	1	1	0
4	0	0	1

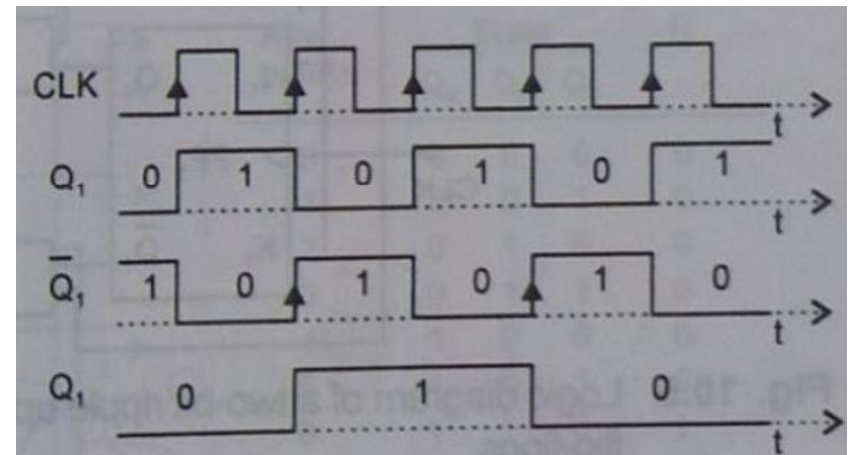




# Digital Logic Circuits




## Ripple/Asynchronous/Serial Counter
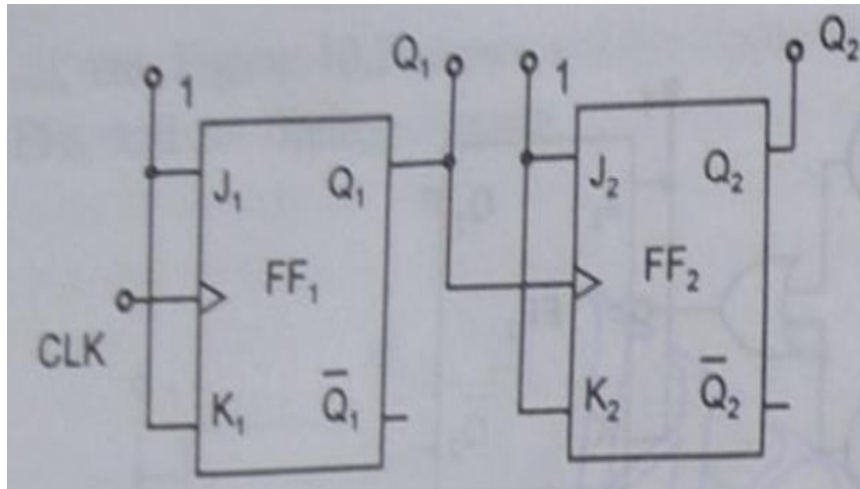
### 2 Bit Positive Edge Triggered Down Counter



Clock Pulse	Q2	Q1
0	0	0
1	1	1
2	1	0
3	0	1
4	0	0

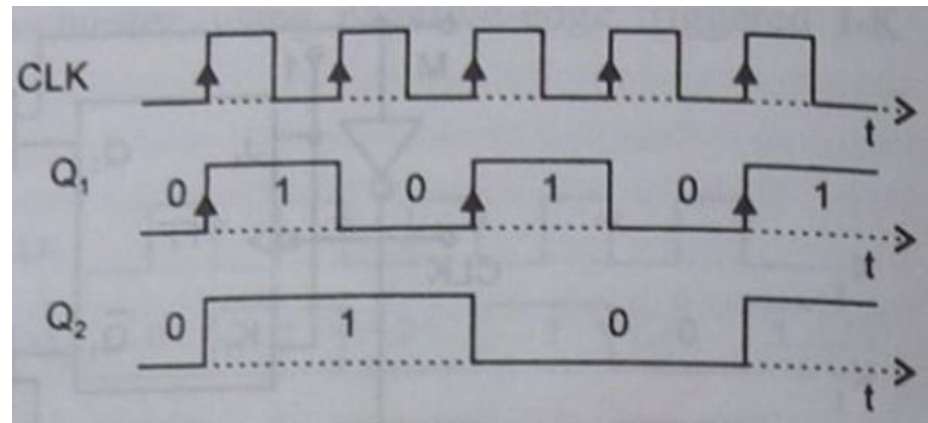




# Digital Logic Circuits



## Ripple/Asynchronous/Serial Counter
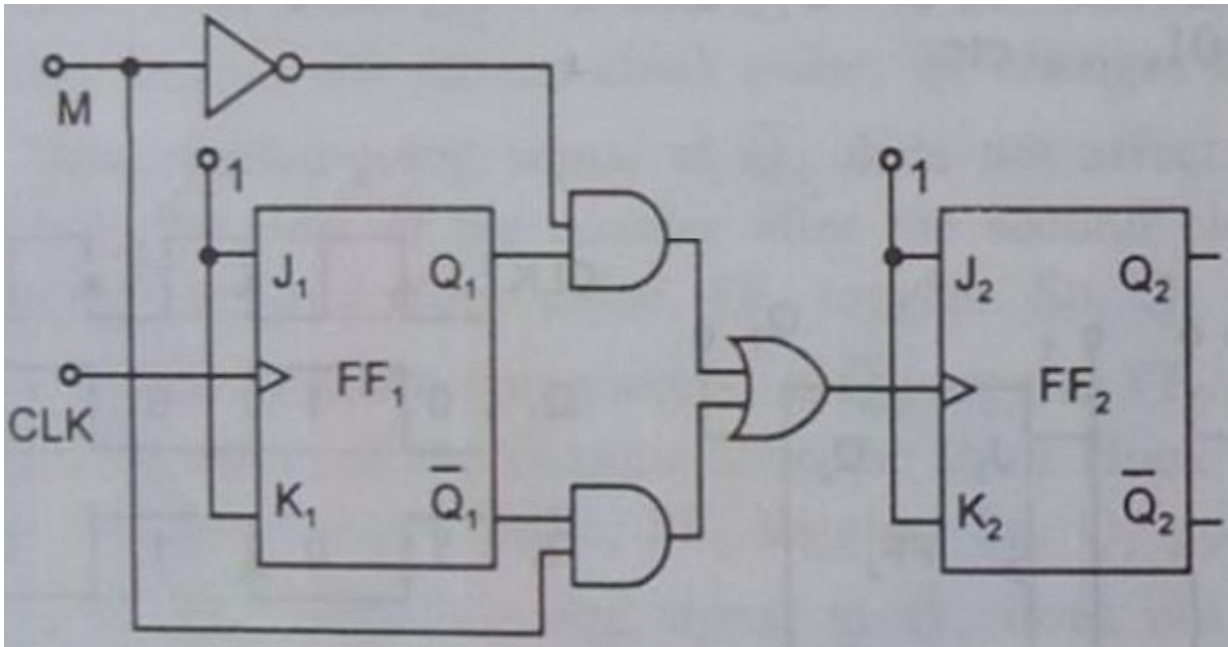
### 2 Bit Positive Edge Triggered UP/Down Counter







# Digital Logic Circuits




## Ripple/Asynchronous/Serial Counter

### Mod 10 Asynchronous Counter Design

After pulses	Count			
	$Q_4$	$Q_3$	$Q_2$	$Q_1$
0	0	0	0	0
1	0	0	0	1
2	0	0	1	0
3	0	0	1	1
4	0	1	0	0
5	0	1	0	1
6	0	1	1	0
7	0	1	1	1
8	1	0	0	0
9	1	0	0	1
10	0	0	0	0

(a) Count table

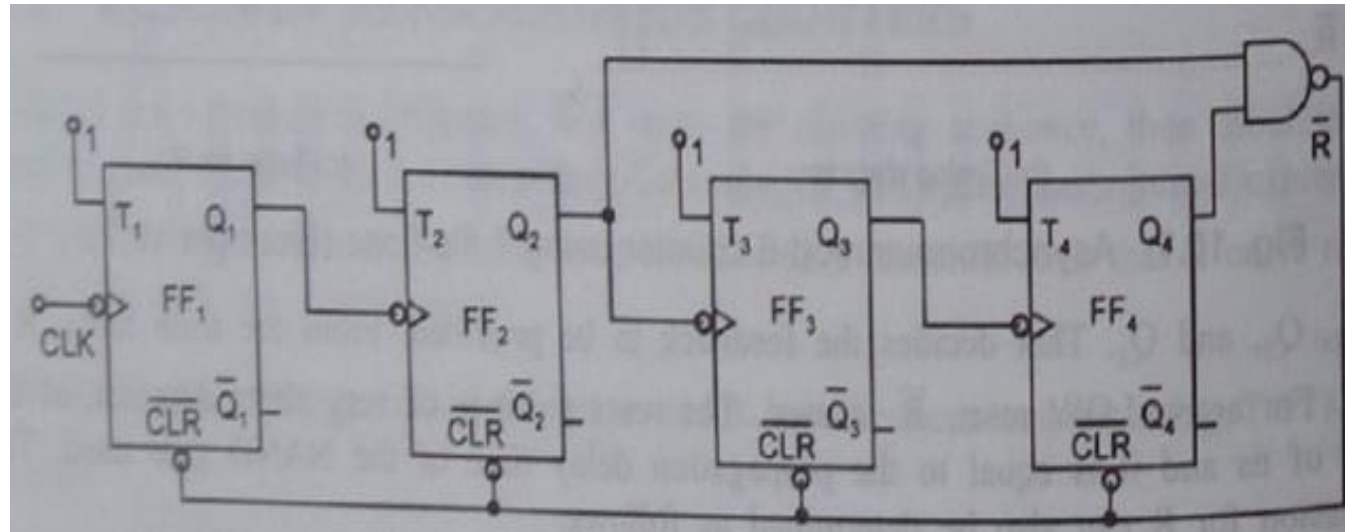






# Digital Logic Circuits



## Synchronous Counter

### 4 Bit UP Counter Design

After clock pulse	State of counter			
	$Q_4$	$Q_3$	$Q_2$	$Q_1$
0	0	0	0	0
1	0	0	0	1
2	0	0	1	0
3	0	0	1	1
4	0	1	0	0
5	0	1	0	1
6	0	1	1	0
7	0	1	1	1
8	1	0	0	0
9	1	0	0	1
10	1	0	1	0
11	1	0	1	1
12	1	1	0	0
13	1	1	0	1
14	1	1	1	0
15	1	1	1	1
16	0	0	0	0
17	0	0	0	1

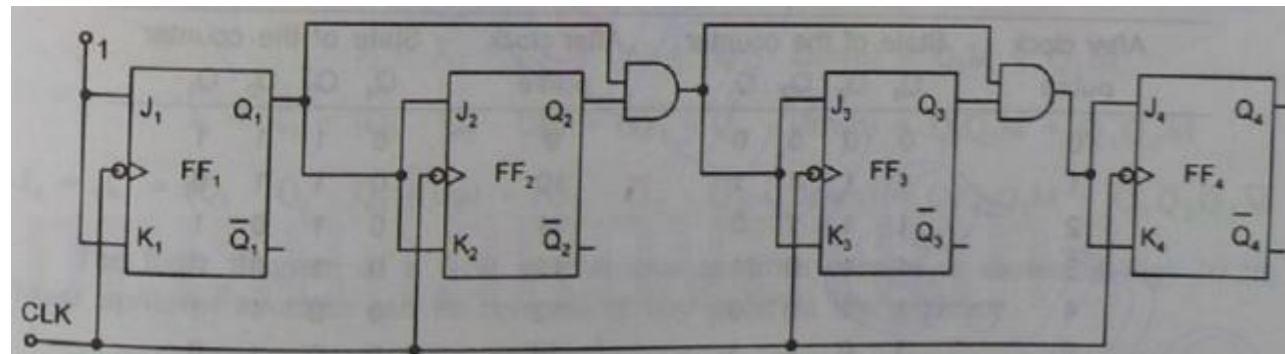






# Digital Logic Circuits



## Synchronous Counter

### 4 Bit Down Counter Design

After clock pulse	State of the counter				After clock pulse	State of the counter			
	$Q_4$	$Q_3$	$Q_2$	$Q_1$		$Q_4$	$Q_3$	$Q_2$	$Q_1$
0	0	0	0	0	9	0	1	1	1
1	1	1	1	1	10	0	1	1	0
2	1	1	1	0	11	0	1	0	1
3	1	1	0	1	12	0	1	0	0
4	1	1	0	0	13	0	0	1	1
5	1	0	1	1	14	0	0	1	0
6	1	0	1	0	15	0	0	0	1
7	1	0	0	1	16	0	0	0	0
8	1	0	0	0	17	1	1	1	1

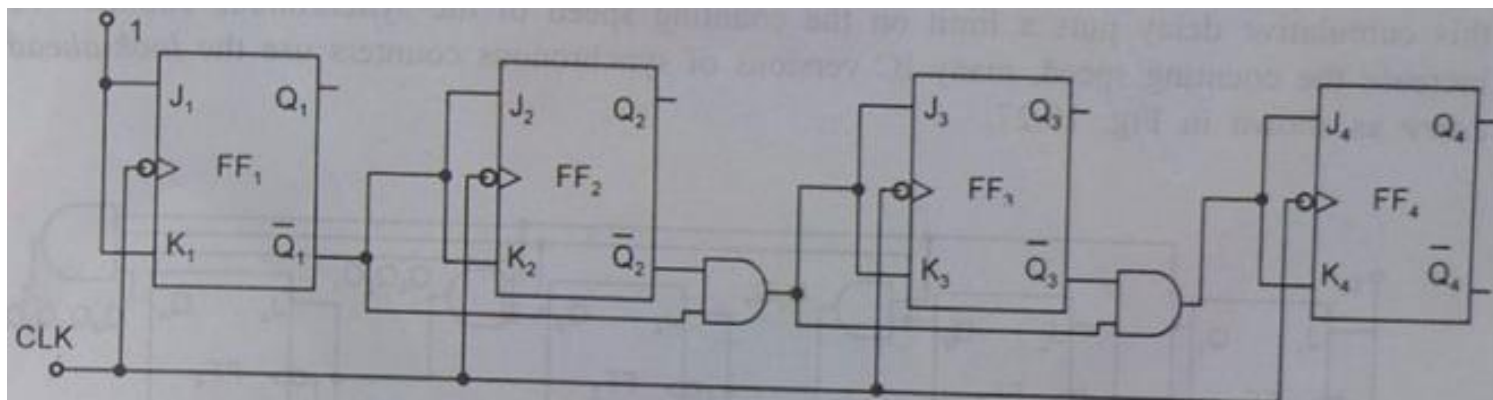




# Digital Logic Circuits



## Ripple/Asynchronous/Serial Counter

### 4 Bit UP/Down Counter Design


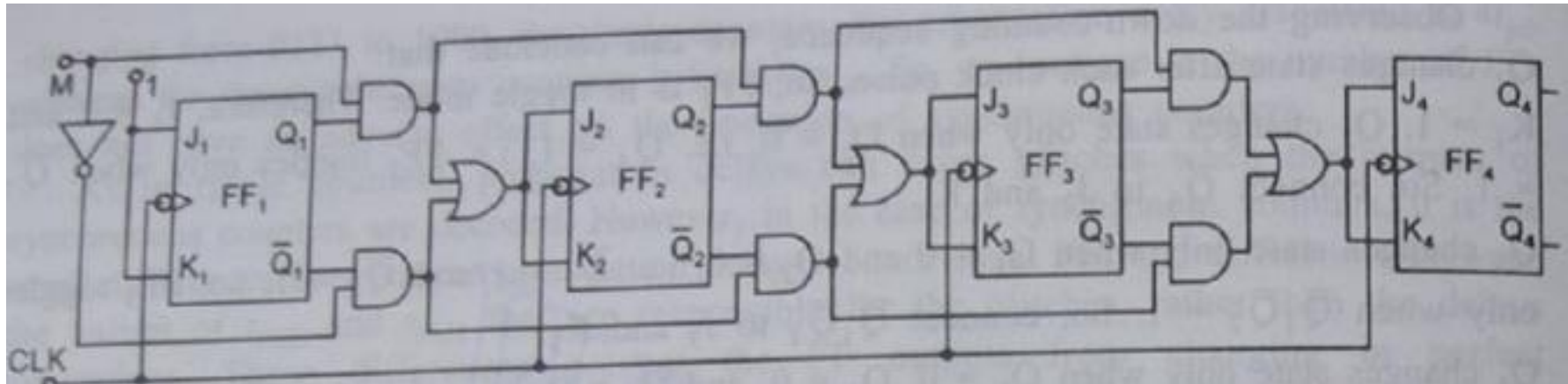




# Digital Logic Circuits



## Ripple/Asynchronous/Serial Counter

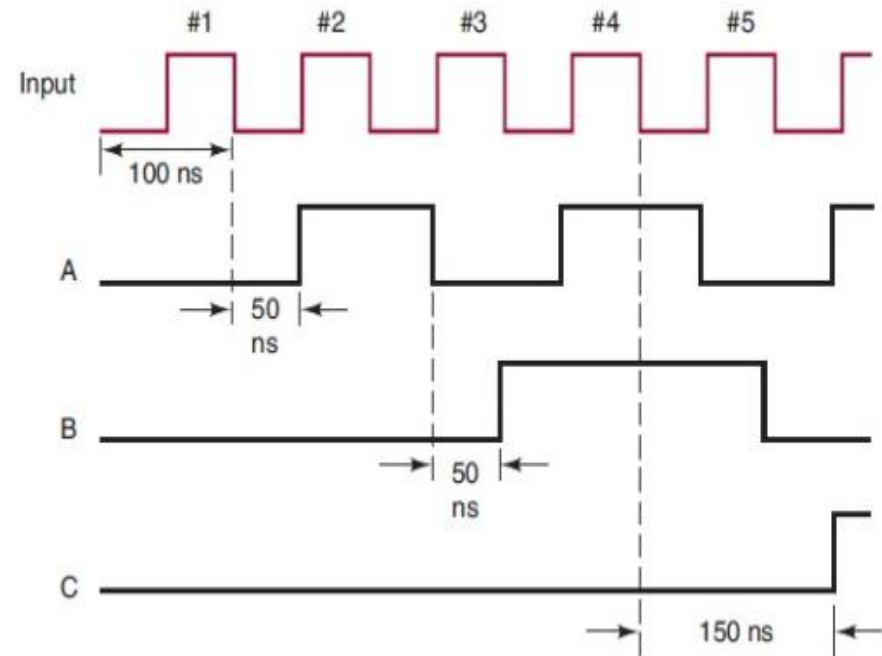 

$$T_{\text{clock}} \geq N \times t_{\text{pd}}$$

$$f_{\text{max}} = \frac{1}{N \times t_{\text{pd}}}$$




# Digital Logic Circuits



A certain J-K flip-flop has  $t_{pd} = 12 \text{ ns}$ . What is the largest MOD counter that can be constructed from these FFs and still operate up to 10 MHz?



# Digital Logic Circuits

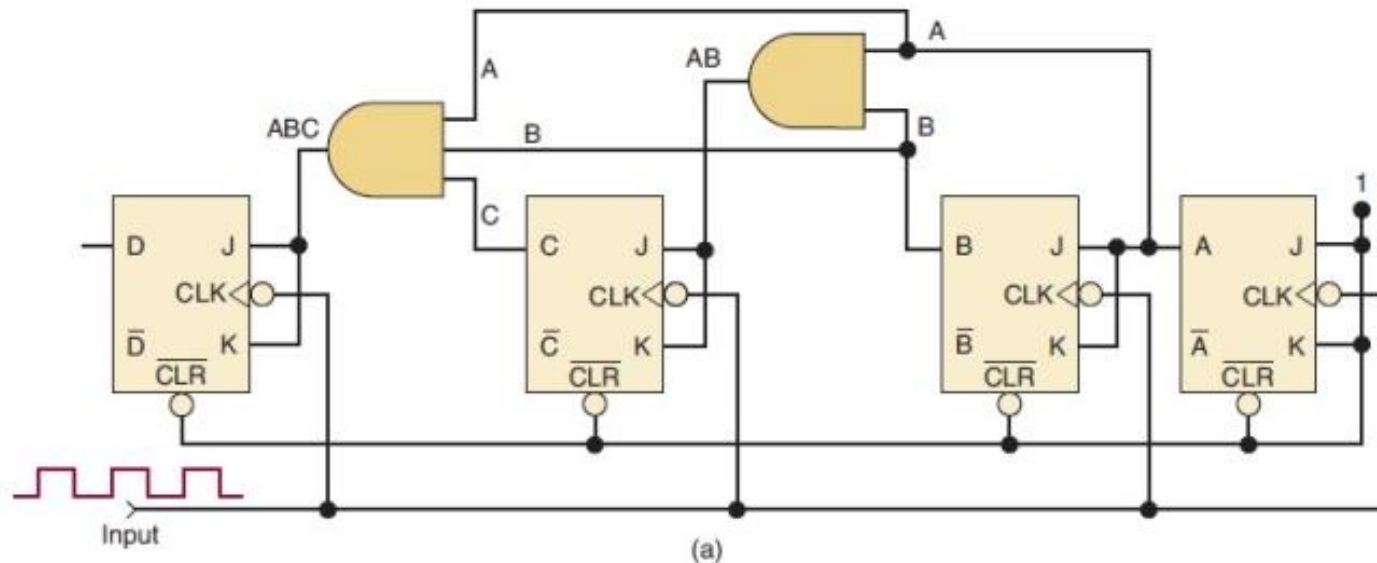

$$\text{total delay} = \text{FF } t_{pd} + \text{AND gate } t_{pd}$$


Determine  $f_{\max}$  for the synchronous counter of Figure above if  $t_{pd}$  for each FF is 50 ns and  $t_{pd}$  for each AND gate is 20 ns. Compare this value with  $f_{\max}$  for a MOD-16 ripple counter.



# Digital Logic Circuits



## State Diagram

 


Present State			Next State		
$Q_2$	$Q_1$	$Q_0$	$Q_2$	$Q_1$	$Q_0$
0	0	0	0	0	1
0	0	1	0	1	1
0	1	1	0	1	0
0	1	0	1	1	0
1	1	0	1	1	1
1	1	1	1	0	1
1	0	1	1	0	0
1	0	0	0	0	0



# Digital Logic Circuits



## Mod 6 Counter

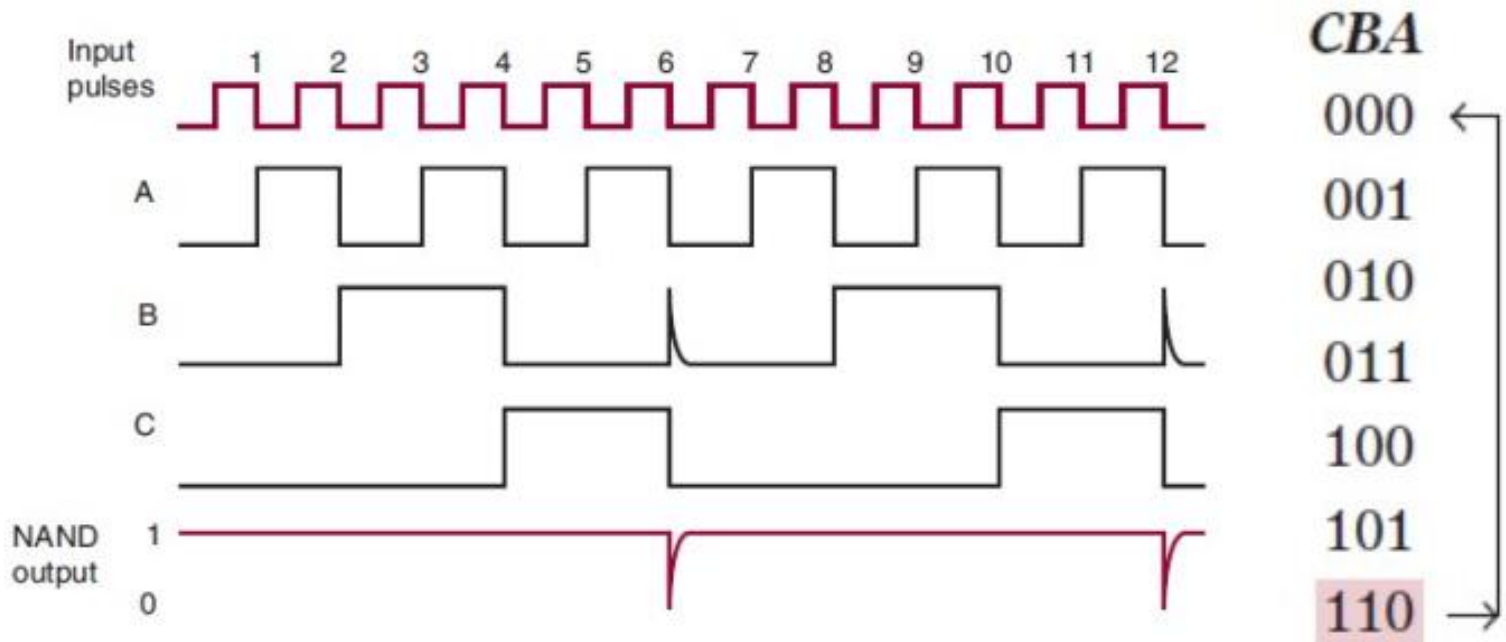






# Digital Logic Circuits



## State Transition Diagram

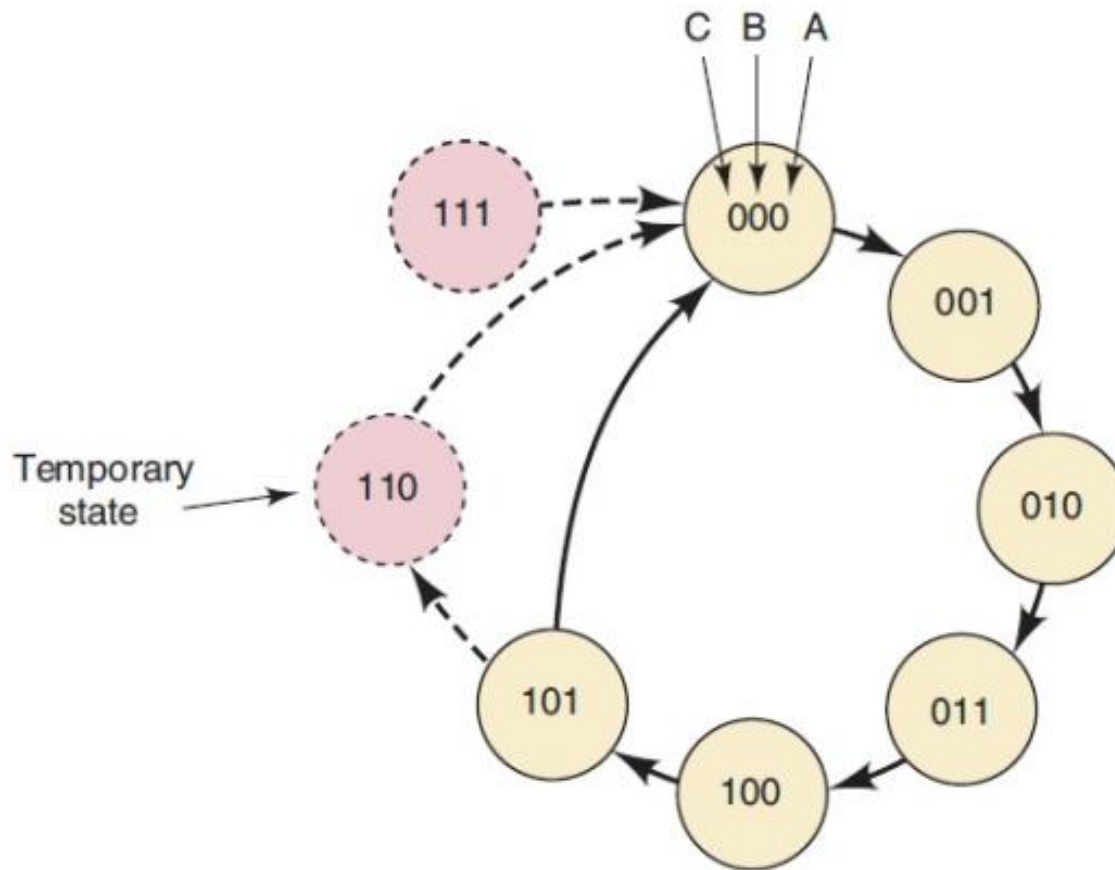



# Digital Logic Circuits



## Synchronous Counter Design


1. Specify the counter sequence and draw a state diagram.
2. Derive a next-state table from the state diagram.
3. Develop a transition table showing the flip-flop inputs required for each transition. The transition table is always the same for a given type of flip-flop.
4. Transfer the  $J$  and  $K$  states from the transition table to Karnaugh maps. There is a Karnaugh map for each input of each flip-flop.
5. Group the Karnaugh map cells to generate and derive the logic expression for each flip-flop input.
6. Implement the expressions with combinational logic, and combine with the flip-flops to create the counter.


 
# Digital Logic Circuits



Design a counter using T Flip-Flops that goes through the states 0-3-5-6-0...



Valid States – 0,3,5,6

Invalid States – 1,2,4,7

PS			NS			Required excitation		
$Q_3$	$Q_2$	$Q_1$	$Q_3$	$Q_2$	$Q_1$	$T_3$	$T_2$	$T_1$
0	0	0	0	1	1	0	1	1
0	1	1	1	0	1	1	1	0
1	0	1	1	1	0	0	1	1
1	1	0	0	0	0	1	1	0

$Q_3 \backslash Q_2 Q_1$	00	01	11	10
0	1	X		X
1	X	1	X	

$T_1 = \overline{Q_2}$

$Q_3 \backslash Q_2 Q_1$	00	01	11	10
0		X	1	X
1	X		X	1


$T_3 = Q_2$

$Q_3 \backslash Q_2 Q_1$	00	01	11	10
0	1	X	1	X
1	X	1	X	1

$T_2 = 1$



# Digital Logic Circuits

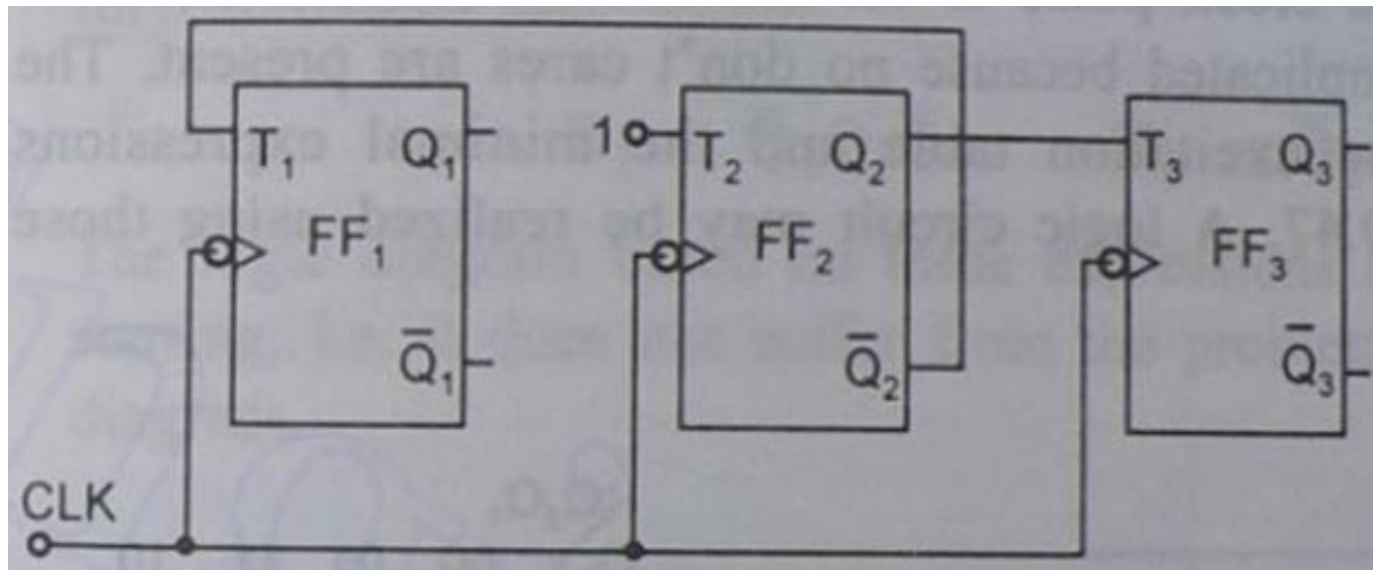




# Digital Logic Circuits



## MOD 6 Counter

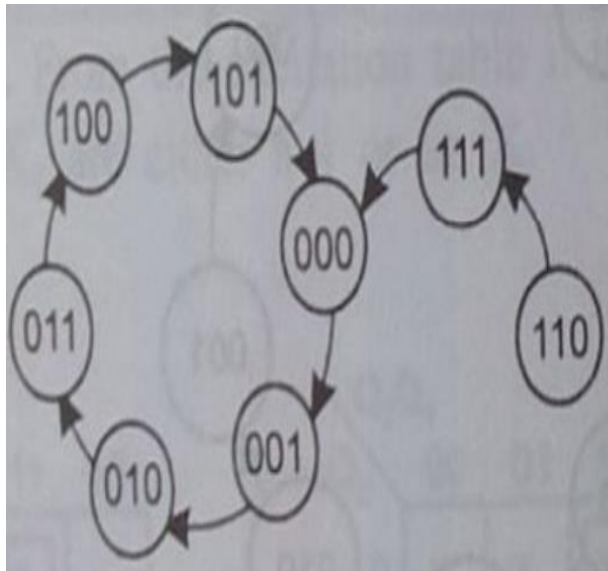


PS			NS			Required excitation					
$Q_3$	$Q_2$	$Q_1$	$Q_3$	$Q_2$	$Q_1$	$J_3$	$K_3$	$J_2$	$K_2$	$J_1$	$K_1$
0	0	0	0	0	1	0	X	0	X	1	X
0	0	1	0	1	0	0	X	1	X	X	1
0	1	0	0	1	1	0	X	X	0	1	X
0	1	1	1	0	0	1	X	X	1	X	1
1	0	0	1	0	1	X	0	0	X	1	X
1	0	1	0	0	0	X	1	0	X	X	1



# Digital Logic Circuits



## MOD 6 Counter

 








# Digital Logic Circuits



## 3 Bit UP Counter

PS			NS			Required excitation					
Q <sub>3</sub>	Q <sub>2</sub>	Q <sub>1</sub>	Q <sub>3</sub>	Q <sub>2</sub>	Q <sub>1</sub>	J <sub>3</sub>	K <sub>3</sub>	J <sub>2</sub>	K <sub>2</sub>	J <sub>1</sub>	K <sub>1</sub>
0	0	0	0	0	1	0	X	0	X	1	X
0	0	1	0	1	0	0	X	1	X	X	1
0	1	0	0	1	1	0	X	X	0	1	X
0	1	1	1	0	0	1	X	X	1	X	1
1	0	0	1	0	1	X	0	0	X	1	X
1	0	1	1	1	0	X	0	1	X	X	1
1	1	0	1	1	1	X	0	X	0	1	X
1	1	1	0	0	0	X	1	X	1	X	1

 





# Digital Logic Circuits



## 3 Bit UP Counter

$Q_2Q_1$		$Q_3$			
		00	01	11	10
$Q_3$	0			1	
	1	X	X	X	X
$J_3 = Q_2Q_1$					

$Q_2Q_1$		$Q_3$			
		00	01	11	10
$Q_3$	0	X	X	X	X
	1			1	
$K_3 = Q_2Q_1$					

$Q_2Q_1$		$Q_3$			
		00	01	11	10
$Q_3$	0		1	X	X
	1		1	X	X
$J_2 = Q_1$					



$Q_2Q_1$		$Q_3$			
		00	01	11	10
$Q_3$	0	X	X	1	
	1	X	X	1	
$K_2 = Q_1$					



# Digital Logic Circuits



## Ring Counter

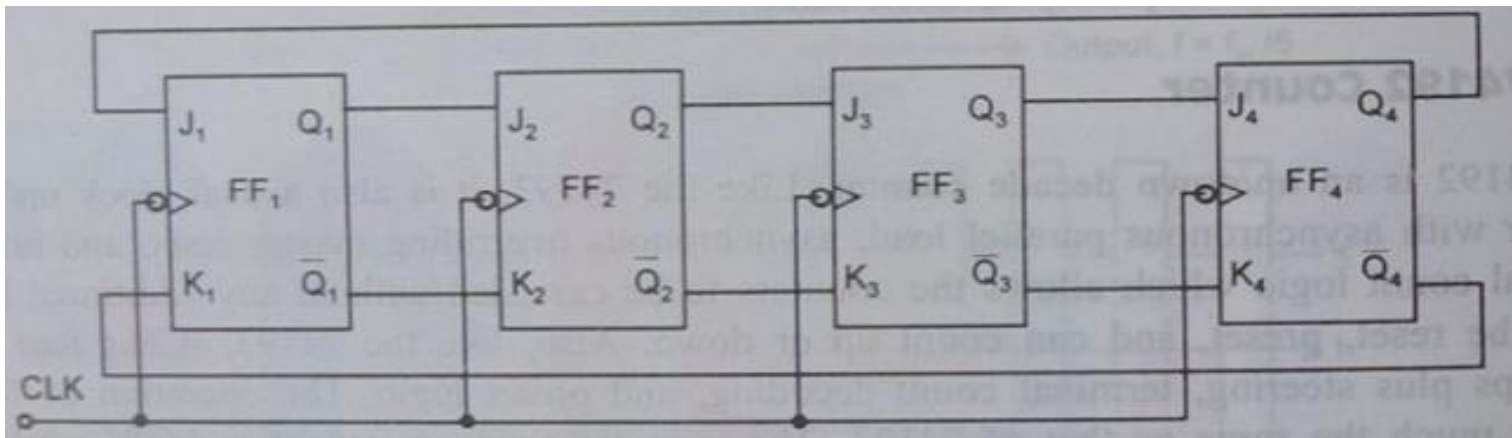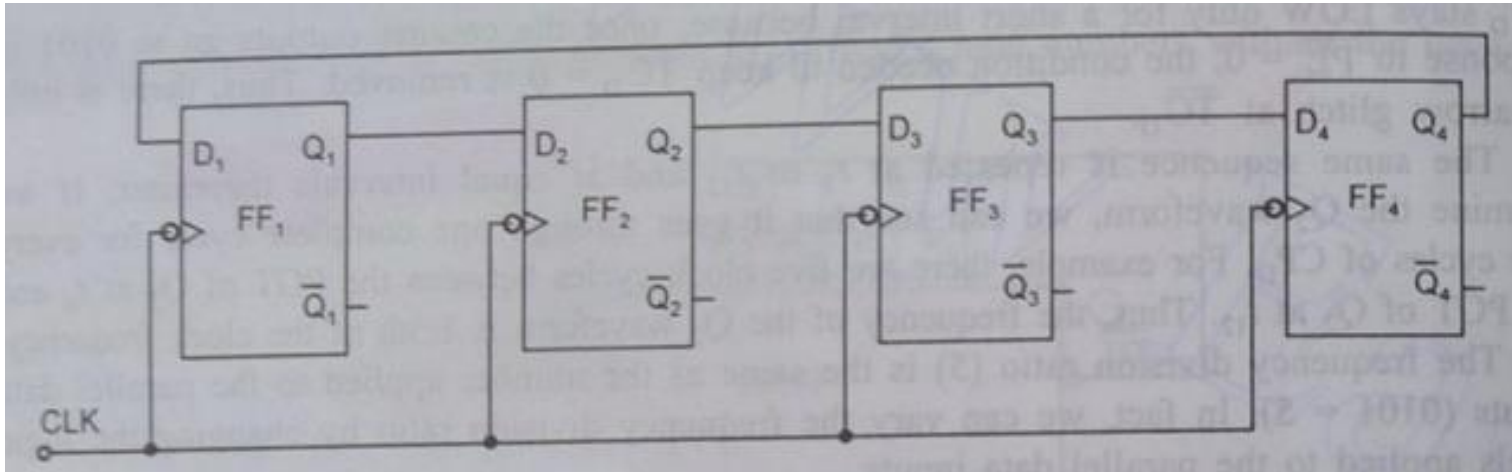




# Digital Logic Circuits



## Ring Counter


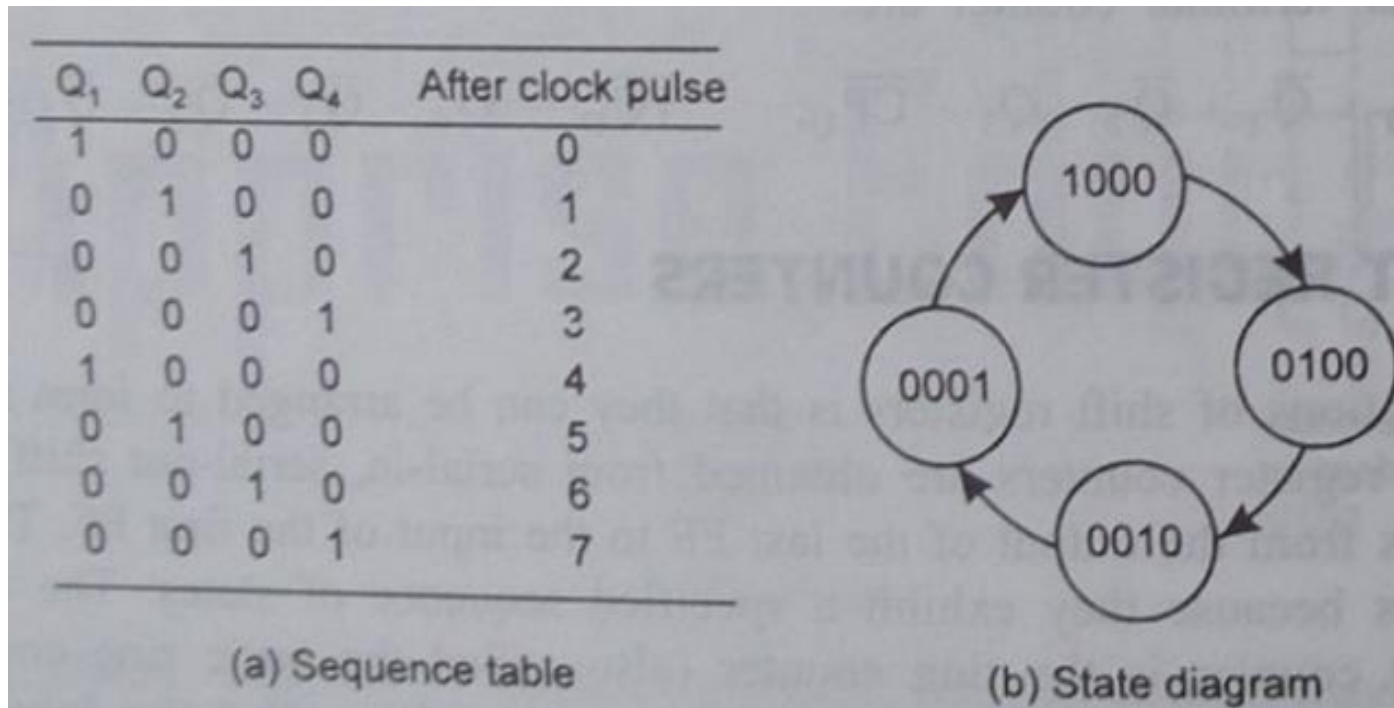




# Digital Logic Circuits


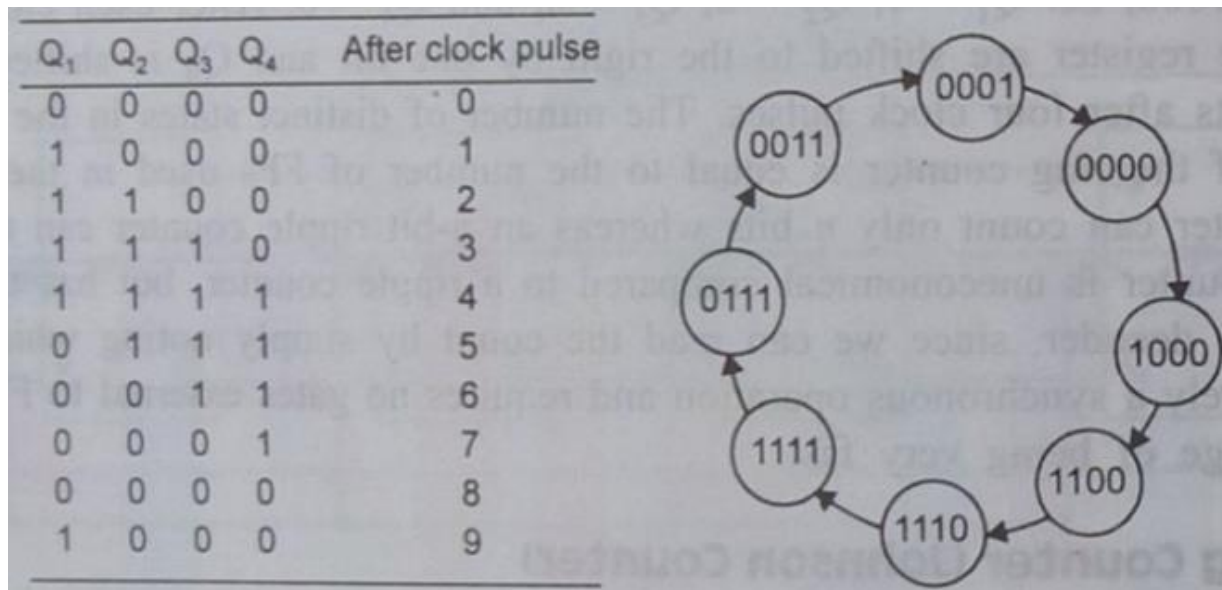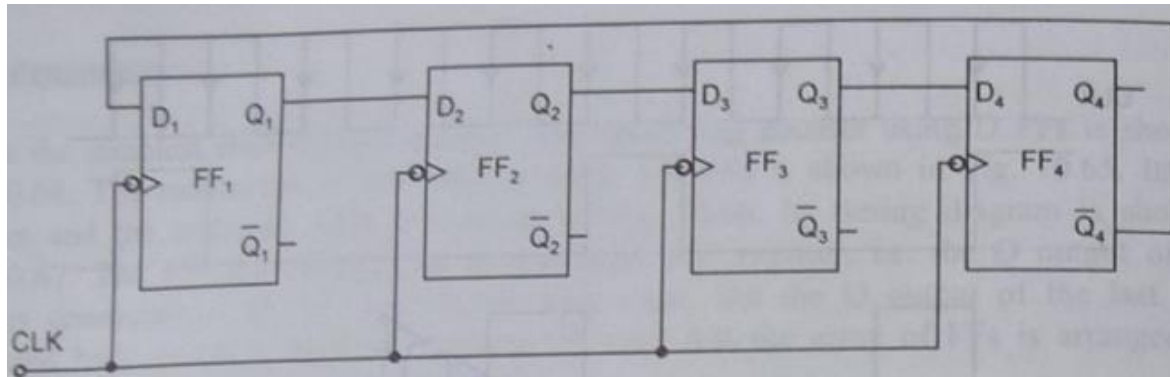
## Johnson Counter or Twisted Ring Counter





# Digital Logic Circuits





# Digital Logic Circuits

