


Dr. Jayesh. M. Dhodiya

Applied Mathematics and Humanities.

Model: IV - LCR Model -

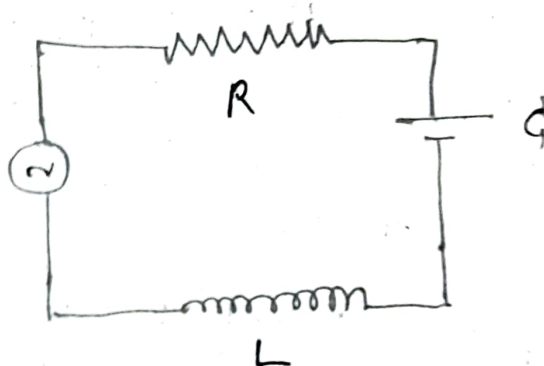* Problem statement

"Consider a series circuit consisting of an EMF source E , a resistor R , a capacitor C and an inductor L . Formulate a suitable differential equation model and analyze it."



* Formulation of model:

Step-I (Identification of Variable)

Here the dependent variable is either the current i or the charge q and the independent variable is the time t .

Step-II (Assumption)

We assume that

- ① The characteristic parameters of the resistor, capacitor and inductor are constant.

(ii) The flow of current in the closed circuit is given by the Kirchhoff's voltage law

$$E_R + E_C + E_L = E \quad \text{--- (1)}$$

Step-III As we know that $E_R = R \cdot i$, $E_L = L \cdot \frac{di}{dt}$,
 $E_C = \frac{q}{C}$ and $i = \frac{dq}{dt}$

we get,

$$E_R + E_C + E_L = E$$

$$\Rightarrow R \cdot i + \frac{q}{C} + L \cdot \frac{di}{dt} = E \quad \text{--- (2)}$$

$$\Rightarrow L \frac{d^2 q}{dt^2} + R \cdot \frac{dq}{dt} + \frac{q}{C} = E \quad \text{--- (3)}$$

[$\because i = \frac{dq}{dt}$]

Again, from eq. (2) we get,

$$R \cdot \frac{di}{dt} + \frac{1}{C} \frac{dq}{dt} + L \frac{d^2 i}{dt^2} = E \quad \text{--- (4)}$$

$$\Rightarrow L \frac{d^2 i}{dt^2} + R \frac{di}{dt} + \frac{1}{C} i = E \quad \text{--- (5)}$$

[$i = \frac{dq}{dt}$]

Eq. (3) and (5) are second order differential equations with single dependent variable representing differential equation model for LCR network.

* Analysis of Mathematical model:

We analyze the LCR model in two steps. In Step-I we obtain the mathematical solution of the

Model and step-II the interpretation of the result obtained. ~~Answer~~ Due to practical impedance we consider following four cases. (2)

Case I LC circuit without voltage source

$$[A=0, B(t)=0]$$

part (I)

From eqn (1) we get,

$$L \frac{d^2 i}{dt^2} + \frac{1}{C} i = 0$$

$$\Rightarrow \frac{d^2 i}{dt^2} + \frac{1}{LC} i = 0$$

$$\Rightarrow \frac{d^2 i}{dt^2} + \omega_0^2 i = 0 \quad \text{--- (2)}$$

$$\text{where } \omega_0^2 = \frac{1}{LC}$$

solution of eqn (2)

A.E is

$$m^2 + \omega_0^2 = 0$$

$$\Rightarrow m = \pm i \omega_0$$

Hence,

$$i(t) = (C_1 \cos \omega_0 t + C_2 \sin \omega_0 t) \quad \text{--- (3)}$$

$$\text{Suppose } C_1 = C \cos \alpha, \quad C_2 = C \sin \alpha$$

$$\Rightarrow C = \sqrt{C_1^2 + C_2^2}, \quad \alpha = \tan^{-1} \left(\frac{C_2}{C_1} \right)$$

$$\Rightarrow i(t) = C \cos \alpha \cos \omega_0 t + C \sin \alpha \sin \omega_0 t$$

$$= C [\cos \alpha \cos \omega_0 t + \sin \alpha \sin \omega_0 t]$$

$$i(t) = C \cos(\omega_0 t - \alpha)$$

Part-III

eq(8) described a simple harmonic motion of period T is given by

$$T = \frac{2\pi}{\omega_0} = 2\pi \sqrt{LC}$$

Its frequency is $\frac{1}{T} = \frac{1}{2\pi\sqrt{LC}}$.


amplitude C and

phase angle α

Case-II

LC - circuit with voltage source

$$CR=0, E(t) \neq 0$$

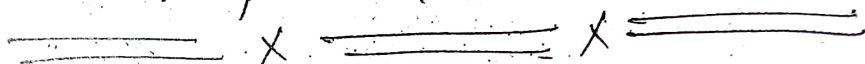

From eq(8) we get,

$$L \frac{d^2 i}{dt^2} + \frac{1}{C} i = E(t)$$

$$\Rightarrow \frac{d^2 i}{dt^2} + \frac{1}{LC} i = \frac{E(t)}{L}$$

$$\Rightarrow \frac{d^2 i}{dt^2} + \omega_0^2 i = \frac{E(t)}{L} \quad \text{--- (9)}$$

$$\text{where } \omega_0^2 = \frac{1}{LC}$$

Suppose $E(t) = E_0 \sin \omega t$ then eq(9) becomes

$$\Rightarrow \frac{d^2 i}{dt^2} + \omega_0^2 i = \frac{E_0 \sin \omega t}{L}$$

$$\Rightarrow \frac{d^2 i}{dt^2} + \omega_0^2 i = \frac{E_0}{L} \cos \omega t \quad \text{where } \omega = \omega_0$$

equation of eq (10)

the solution of eq (10) is given by

$$i(t) = i_c(t) + i_p(t)$$

(3)

For $i_c(t)$

A.E

$$\frac{d^2 i}{dt^2} + \omega_0^2 i = 0$$

A.E

$$\omega^2 + \omega_0^2 = 0$$

$$\Rightarrow i_c(t) = C_1 \cos \omega_0 t + C_2 \sin \omega_0 t$$

Suppose $C_1 = C \cos \phi$, $C_2 = C \sin \phi$ then

$$i_c(t) = C \cos(\omega_0 t - \phi) \quad \text{where } \phi = \tan^{-1} \left(\frac{C_2}{C_1} \right)$$

For $i_p(t)$

$$i_p(t) = \frac{1}{(\beta^2 + \omega^2)} F_0 \cos \omega t$$

$$= F_0 \frac{1}{\beta^2 + \omega^2} \cos \omega t$$

When $\omega \neq \omega_0$ then

$$i_p(t) = F_0 \frac{1}{-\omega^2 + \omega_0^2} \cos \omega t$$

$$\Rightarrow i_p(t) = \frac{F_0}{\omega_0^2 - \omega^2} \cos \omega t \quad \text{--- (11)}$$

When $\omega = \omega_0$ then

$$i_p(t) = F_0 \cdot \frac{1}{2\beta} \cos \omega t$$

$$= \frac{F_0}{2} \frac{\sin \omega t}{\omega}$$

$$\left[\frac{1}{\beta^2 + \omega^2} = \frac{1}{2\beta} \right]$$

$$i_p(t) = F_0 \left(\frac{1}{2\omega} \right) \sin \omega t$$

Thus, the general solution is given by

$$i(t) = i_c(t) + i_p(t)$$

$$\Rightarrow i(t) = C \cdot \cos(\omega_0 t - \alpha) + \frac{F_0 \cos \omega t}{\omega_0^2 - \omega^2} \quad [\omega \neq \omega_0] \quad (13)$$


$$i(t) = C \cdot \cos(\omega_0 t - \alpha) + F_0 \cdot \left(\frac{1}{2\omega_0} \right) \sin \omega t \quad (14)$$

Post-II Interpretation

From eq(13) it is clear that the resulting motion is the superposition of two oscillation one with natural circular frequency ω_0 and the other with external circular frequency ω .

From eq(14) it is clear that the resulting motion is the reinforcement of the natural vibrations of the system given by $\cos(\omega_0 t - \alpha)$ by externally impressed vibrations at the same frequency ω_0 but by every increasing amplitude given by $\left(\frac{F_0}{2\omega_0} \right) t \sin \omega t$. The

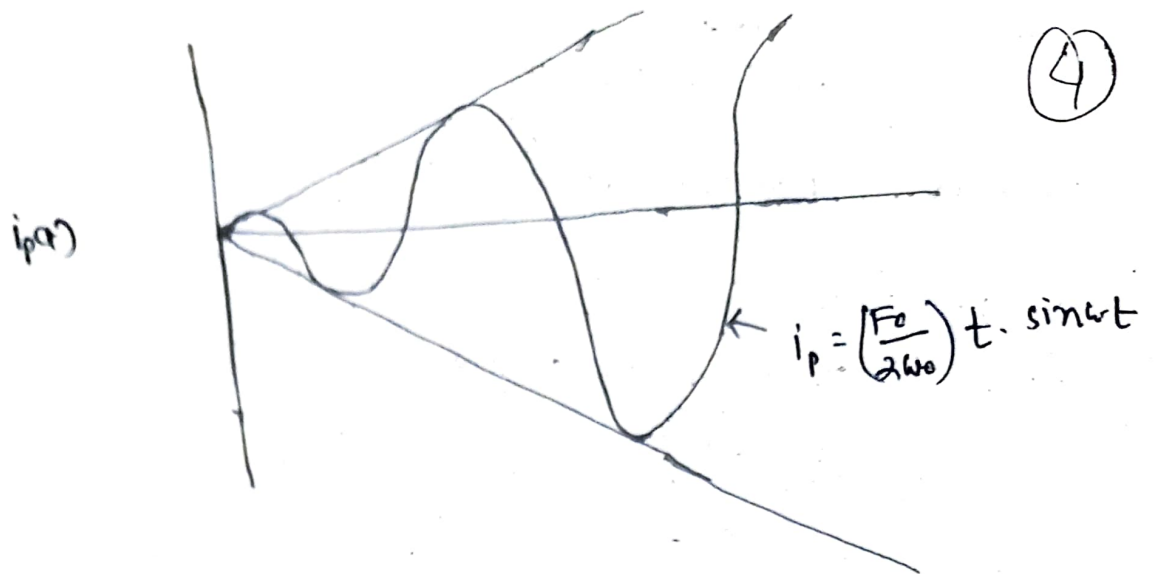graph of $i(t)$ given below shows clearly how the amplitude of the oscillations theoretically ~~in~~ increase without limit in the case $\omega = \omega_0$.



Exe - III

LCR - Network without voltage source ($E(t) = 0$)

From eq(5) we get.

$$L \frac{d^2 i}{dt^2} + R \frac{di}{dt} + \frac{1}{C} i = 0$$

$$\Rightarrow \frac{d^2 i}{dt^2} + \frac{R}{L} \frac{di}{dt} + \frac{1}{LC} i = 0$$

$$\Rightarrow \frac{d^2 i}{dt^2} + 2p \frac{di}{dt} + \omega_0^2 i = 0$$

where $2p = \frac{R}{L}$, $\omega_0^2 = \frac{1}{LC}$

solution of eq(15)

The auxiliary equation of

$$\frac{d^2 i}{dt^2} + 2p \frac{di}{dt} + \omega_0^2 i = 0 \text{ is}$$

$$m^2 + 2p m + \omega_0^2 = 0,$$

whose roots are m_1 and m_2 are given by

$$m_1 = -p + \sqrt{p^2 - \omega_0^2} \quad \text{cases a-d}$$

$$m_2 = -p - \sqrt{p^2 - \omega_0^2}$$

We note that s_1, s_2 are real and distinct, referred as complex conjugate according as

$$p^2 \begin{matrix} > \\ = \\ < \end{matrix} \omega_0^2$$

$$\Rightarrow \left(\frac{R}{2L}\right)^2 \begin{matrix} > \\ = \\ < \end{matrix} \frac{1}{LC} \quad \left[\because p = \frac{R}{2L}, \omega_0^2 = \frac{1}{LC} \right]$$

$$\Rightarrow \frac{R}{2L} \begin{matrix} > \\ = \\ < \end{matrix} \frac{1}{\sqrt{LC}}$$

$$\Rightarrow R \begin{matrix} > \\ = \\ < \end{matrix} 2\sqrt{L/C} \quad \text{--- (16)}$$

Let us set $2\sqrt{L/C} = R_c$ and designate it as a critical path resistance.

IF $R > R_c$ [Overdamped Case]

Then m_1 and m_2 are real and distinct roots. Hence

$$i(t) = A e^{m_1 t} + B e^{m_2 t} \quad \text{--- (17)}$$

where A and B are arbitrary constant.

IF $R = R_c$ [Critically damped case]

Then $m_1 = m_2 = -p$, Hence

$$i(t) = (A + B.t) e^{-pt} \quad \text{--- (18)}$$

IF $R < R_c$ (Underdamped case)

(5)

Then the roots are complex conjugate given

by $M_1 = -p + i\sqrt{\omega_0^2 - p^2},$

$M_2 = -p - i\sqrt{\omega_0^2 - p^2}$

Hence,

~~$i(t) = e^{-pt} (C_1 \cos \omega_1 t + C_2 \sin \omega_1 t)$~~

$i(t) = e^{-pt} (A \cos(\sqrt{\omega_0^2 - p^2} t) + B \sin(\sqrt{\omega_0^2 - p^2} t))$

$i(t) = e^{-pt} (A \cos \omega_1 t + B \sin \omega_1 t)$ (19)

where

$\omega_1 = \sqrt{\omega_0^2 - p^2}$

$= \sqrt{\frac{1}{LC} - \frac{R^2}{4L^2}}$

if we take

$A = C \cos \phi, \quad B = C \sin \phi$

$\Rightarrow i(t) = C e^{-pt} (\cos \phi \cos \omega_1 t + \sin \phi \sin \omega_1 t)$

$i(t) = C e^{-pt} \cos(\omega_1 t - \phi)$ (20)

where $C = \sqrt{A^2 + B^2}$

$\tan \phi = (B/A) \Rightarrow \phi = \tan^{-1}(B/A)$

(II) Interpretation


① $R > R_c$ (Overdamped case)

From (17) it is clear that as $t \rightarrow \infty$

$i(t) \rightarrow 0$

Thus, the system settles to its equilibrium position without any oscillations.

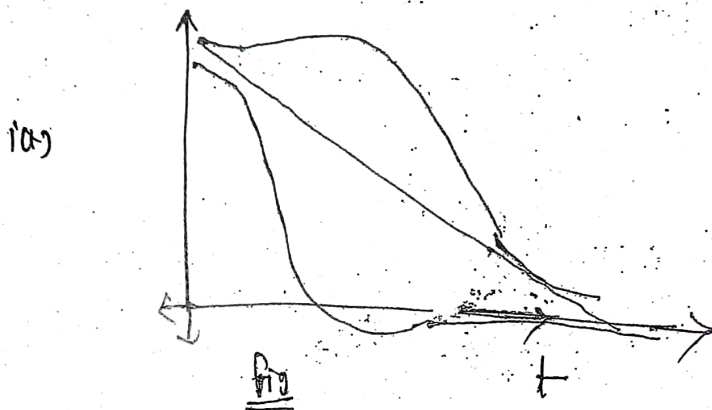We choose $i(0) = 1$ a fixed positive number as the initial point and illustrate the effects of changing the initial slope $i'(0)$. We notice that in every case there would be oscillations which are damped out



(2) $R = R_c$ [Critically damped case]

From eq (18) we note the following facts.


(a) As $t \rightarrow \infty$, $i(t) \rightarrow 0$

(b) since $\frac{-b}{2} > 0$ and $(A+Bt)$ has almost the positive zero therefore the system passes through its equilibrium position almost once. The graph in this case is similar to that as in (1).

③ $R < R_c$

eq. (23) represents exponentially damped oscillation of the system about its equilibrium position. The graph of it lies between the curve $i(t) = c e^{-bt}$ and $i(t) = -c e^{-bt}$ (\because Range of \cos is $[-1, 1]$).

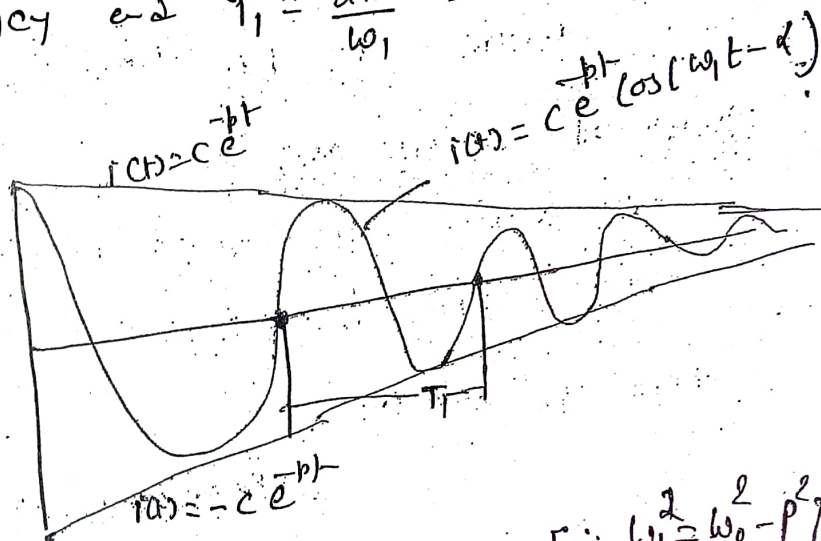In this case the motion is said to be pseudoperiodic with $c e^{-bt}$ as its time varying amplitude, ω_1 as its circular frequency and $T_1 = \frac{2\pi}{\omega_1}$ as its pseudo-period.



Further we note that $\omega_1 < \omega_0$ [$\because \omega_1^2 = \omega_0^2 - p^2$]
therefore $T_1 > T$

Thus, the damp exhibits the following three effects.

- It exponentially damps the oscillation according to the time varying amplitude.
- It slows the motion (since $\omega_1 < \omega_0$).
- It delays the motion.

Case-IV LCR Model with Voltage Source. & *

(I) From equation (5) we get,

$$L \frac{d^2 i}{dt^2} + R \frac{di}{dt} + \frac{1}{C} i = E' \quad (21)$$

Suppose $E(t) = E_0 \sin \omega t$, then (21) becomes

$$\frac{d^2 i}{dt^2} + \frac{R}{L} \frac{di}{dt} + \frac{1}{LC} i = \frac{E_0 \omega}{L} \cos \omega t$$

$$\Rightarrow \frac{d^2 i}{dt^2} + 2p \frac{di}{dt} + \omega_0^2 i = F_0 \cos \omega t \quad (22)$$

$$\text{where } 2p = \frac{R}{L}, \quad \omega_0^2 = \frac{1}{LC}, \quad F_0 = \frac{E_0 \omega}{L}$$

Solution of equation (22)

The solution of (22) is obtained as

$$i(t) = i_c(t) + i_p(t)$$

from the case (3)

$$i_c(t) = c e^{-pt} \cos(\omega_0 t - \alpha) \quad (23)$$

For particular integral

$$i_p(t) = \frac{1}{\omega^2 + 2p\omega + \omega_0^2} F_0 \cos \omega t$$

$$= F_0 \frac{1}{[2p\omega + \omega^2 - \omega_0^2]} \cos \omega t$$

$$= F_0 \frac{1}{(2p\omega - (\omega^2 - \omega_0^2))} \cos \omega t$$

$$= F_0 \frac{1}{(2PD - (\omega^2 - \omega_0^2)) \times (2PD + (\omega^2 - \omega_0^2))} \cos \omega t \quad (7)$$

$$= F_0 \frac{(2PD + (\omega^2 - \omega_0^2))}{[4P^2D^2 - (\omega^2 - \omega_0^2)^2]} \cos \omega t.$$

$$= \frac{F_0}{[4P^2D^2 - (\omega^2 - \omega_0^2)^2]} [-2PD \sin \omega t - (\omega_0^2 - \omega^2) \cos \omega t]$$

$$= \frac{F_0}{4P^2D^2 + (\omega^2 - \omega_0^2)^2} [2PD \sin \omega t + (\omega_0^2 - \omega^2) \cos \omega t] \quad (24)$$

Now, putting $2PD = \epsilon \cos \phi$ and $\omega_0^2 - \omega^2 = -\epsilon \sin \phi$

in eq (24)

We get

$$i_p(t) = \frac{F_0}{4P^2D^2 + (\omega_0^2 - \omega^2)^2} \times [\epsilon \cos \phi \sin \omega t - \epsilon \sin \phi \cos \omega t]$$

$$i_p(t) = \frac{F_0}{4P^2D^2 + (\omega_0^2 - \omega^2)^2} \epsilon \sin(\omega t - \phi) \quad (25)$$

$$\Rightarrow i_p(t) = I_0 \sin(\omega t - \phi) \quad (26)$$

where $I_0 = \frac{F_0}{4P^2D^2 + (\omega_0^2 - \omega^2)^2}$

Hence, solution is

$$i(t) = i_c(t) + i_p(t)$$

II Interpretation

Notwithstanding the specific form of $i(t)$ that is, whether it is given by eq. (12), (18) or (21) we note that $i(t) \rightarrow 0$ at $t \rightarrow \infty$, thus $I_a(t)$ as a transient solution and gives the transient current which dies out with the passage of time.

From eq (21), it is clear that $i_p(t)$ represent the simple Harmonic motion of period $2/\omega$ and amplitude $E_0/2$.

The Expression for $i_p(t)$, being a sine term of constant amplitude, continue to contribute to the motion in periodic, oscillatory manner. Thus $i_p(t)$ gives the steady periodic current.
