## **Assignment 5**

Garvit Shah U21CS089

## Design circuit for 1 bit ALU that performs SUB, NAND and NOR operations in logisim simulation tool







