

Assignment 6

Garvit Shah
U21CS089

Design a circuit to multiply two Arrays of 4 bits and 3 bits.

Follow this formula to build the circuit: If multiplicand = k bits, multiplier = j bits then $(j * k)$ AND

gates and $(j-1)$ k bit adders are required to produce a result. Use your own adders to build the circuits.



