


# Experiment : 3

Date \_\_\_\_\_  
Page \_\_\_\_\_


Aim : Verification of superposition theorem for electric circuit.

Apparatus : DC power supply, Ammeter (0-2A), Voltmeter (0-150 V), Rheostat, Multimeter.


Circuit diagram :

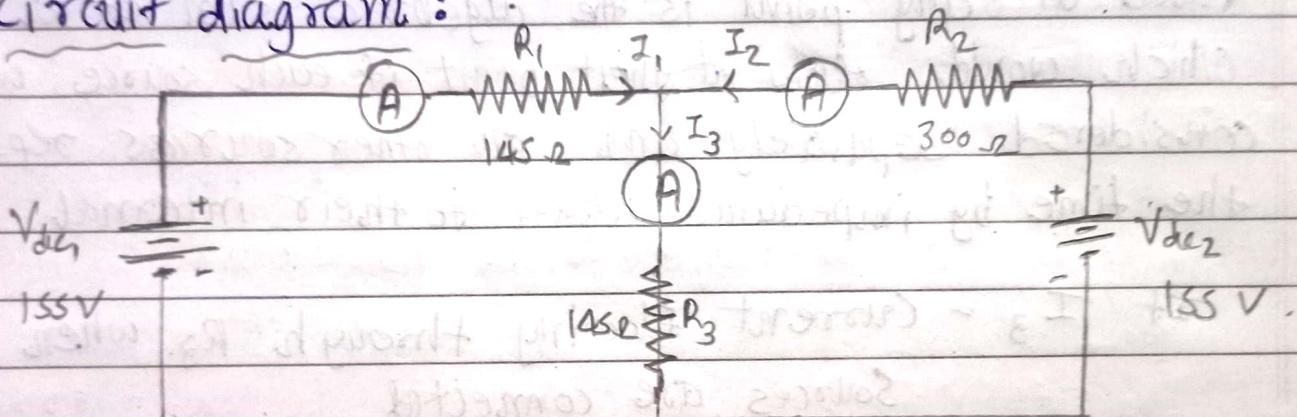

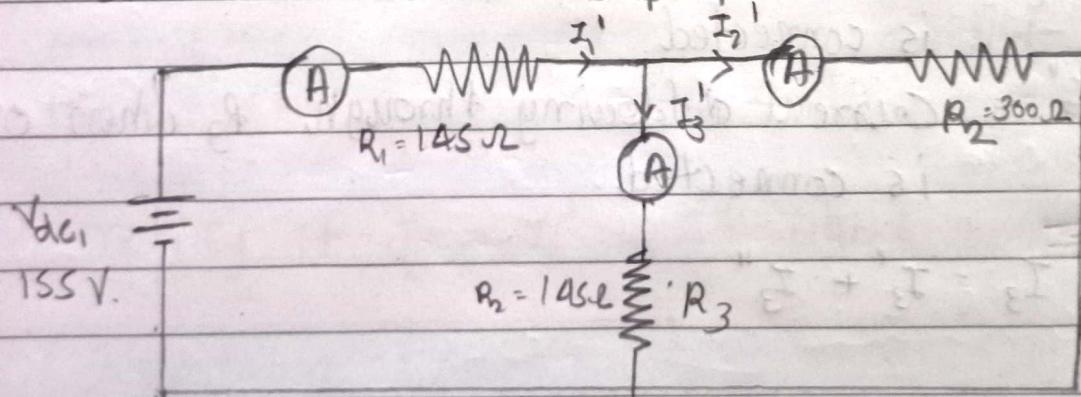Resistive circuit for superposition theorem



Resistive circuit with  $V_{dc1} = 155V$

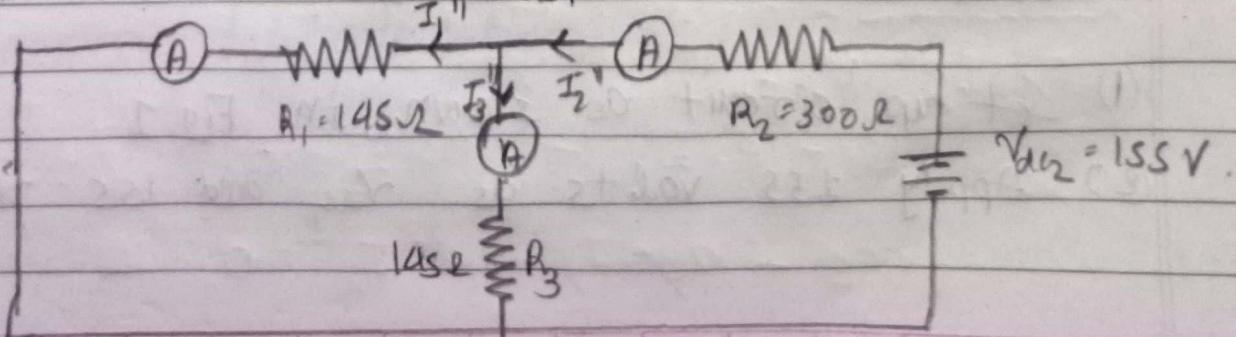

E:\Downloads\Ex

Theory :

If network contains two or more than two sources, then principle of superposition theorem is used to simplify network calculations. It may be stated as follow "In a bilateral network if two or more than two energy sources are present, then the current flows at any point is the algebraic sum of all currents which would flow at that point if each source was considered separately and all other sources replaced at the time by impedance equal to their internal impedances.

If  $I_3$  = Current flowing through  $R_3$  when both sources are connected

$I_3'$  = Current flowing through  $R_3$  when only  $V_{dc}$  is connected.

$I_3''$  = Current flowing through  $R_3$  when only  $V_{ac}$  is connected.

then,

$$I_3 = I_3' + I_3''$$

Procedure :

- (1) Set up circuit as shown in Fig. 1
- (2) Apply 155 volts as  $V_{dc}$  and 155 volts as  $V_{ac}$

- (3) Measure the current  $I_1, I_2, I_3$  using ammeters connected in the circuit and note it in table.
- (4) Now, short circuit the terminal where  $V_{dc2}$  is connected as shown in Fig. 2.
- (5) Measure the current  $I'_1, I'_2$ , and  $I'_3$  using ammeters connected in the circuit and note it in table.
- (6) Now short circuit the terminal where  $V_{dc1}$  is connected and apply 155V to  $V_{dc2}$  terminal as shown in Fig. 3.
- (7) Measure the current  $I''_1, I''_2$ , and  $I''_3$  using ammeters connected in the circuit and note it in table
- (8) Verify if  $I_3 = I'_3 + I''_3$  which would

Observation :

(1) Experimental calculations :

## Current through resistors

$V_{dc_1} = 155 V$	$V_{dc_1} = 155 V$	$V_{dc_1} = 0 V$
$V_{dc_2} = 155 V$	$V_{dc_2} = 0 V$	$V_{dc_2} = 155 V$
$I_1 = 0.5 A$	$I_1' = 0.7 A$	$I_1'' = 0.24 A$
$I_2 = 0.23 A$	$I_2' = 0.23 A$	$I_2'' = 0.45 A$
$I_3 = 0.7 A$	$I_3' = 0.5 A$	$I_3'' = 0.24 A$

## (2) mathematical calculations:

### Current through resistors.

$V_{dc_1} = 155 V$	$V_{dc_1} = 155 V$	$V_{dc_1} = 0 V$
$V_{dc_2} = 155 V$	$V_{dc_2} = 0 V$	$V_{dc_2} = 155 V$
$I_1 = 0.43$	$I_1' = 0.64$	$I_1'' = 0.21$
$I_2 = 0.21$	$I_2' = 0.21$	$I_2'' = 0.42$
$I_3 = 0.64$	$I_3' = 0.43$	$I_3'' = 0.21$

### Calculations :

For Fig. 1.

Apply KVL

$$155 - 145 I_1 - 145 I_3 = 0 \quad (\because I_3 = I_1 + I_2)$$

$$\therefore 155 - 290 I_1 - 145 I_2 = 0 \quad @$$

$$155 - 145 I_1 + 300 I_2 - 155 = 0.$$

$$145 I_1 - 300 I_2 = 0 \quad \text{--- (2)}$$

$\text{eq. } (1) \times 2 + \text{eq. } 2$  so we get

$$155 - 290 I_1 - 145 I_2 + 290 I_1 - 600 I_2 = 0.$$

$$I_2 = \frac{155}{745} = 0.208.$$

$$I_2 = 0.21A.$$

From eq. (2).  $I_1 = \frac{300(0.21)}{145}$

$$I_1 = 0.43A.$$

and  $I_3 = I_1 + I_2 = 0.43 + 0.21$

$$I_3 = 0.64A.$$

For Fig-2.

$$R_{\text{eq}} = R_1 + \frac{R_2 R_3}{R_2 + R_3} = 145 + \frac{300 \times 145}{445}$$

$$R_{\text{eq}} = 242.75.$$

$$I_1' = \frac{V_{\text{dc}}}{R_{\text{eq}}} = \frac{155}{242.75} = 0.638 = 0.64.$$

$$I_1' = 0.64A$$

$$I_2' = I_1' \times \frac{R_3}{R_2 + R_3} = \frac{0.64 \times 145}{445} = 0.21$$

$$I_2' = 0.21 \text{ A.}$$

$$I_3' = I_1' - I_2' = 0.64 - 0.21 = 0.43.$$

$$I_3' = 0.43 \text{ A}$$

For Fig-3

$$R_{eq} = \frac{R_2 + R_1 R_3}{R_1 + R_3} = \frac{300 + \frac{145 \times 145}{290}}{290} = 300 + 72.5.$$

$$R_{eq} = 372.5 \Omega.$$

$$I_2'' = \frac{V_{dc2}}{R_{eq}} = \frac{155}{372.5} = 0.416 \approx 0.42.$$

$$I_2'' = 0.42 \text{ A}$$

As  $R_1$  and  $R_3$  has equal resistance so the current will be divided equally,

$$I_1'' = I_3'' = \frac{0.42}{2} = 0.21$$

$$I_1'' = 0.21 \text{ A} \quad I_3'' = 0.21 \text{ A}$$

Now, let's verify superposition theorem.

for  $I_1$ 

$$I_1 = I_1' - I_1''$$

$$\text{L.H.S. } I_1 = 0.43$$

$$\text{R.H.S.} = I_1' - I_1'' = 0.64 - 0.21 = 0.43$$

$$\text{L.H.S.} = \text{R.H.S.}$$

For  $I_2$ 

$$I_2 = I_2'' - I_2'$$

$$\text{L.H.S.} = I_2 = 0.21$$

$$\text{R.H.S.} = I_2'' - I_2' = 0.42 - 0.21 = 0.21$$

$$\therefore \text{L.H.S.} = \text{R.H.S.}$$

For  $I_3$ 

$$I_3 = I_3' + I_3''$$

$$\text{L.H.S.} = I_3 = 0.64.$$

$$\text{R.H.S.} = I_3' + I_3'' = 0.21 + 0.43 = 0.64.$$

$$\therefore \text{L.H.S.} = \text{R.H.S.}$$

Hence superposition theorem is valid.

Question:

Q) What are the limitations of superposition theorem?

- It cannot be used to measure power.
- It is valid only for linear and bilateral network.
  - It can only be used for circuits having two or more than two energy sources.
  - This theorem is not applicable to unbalanced bridge circuits.

Result :

For fig-1,

The current through resistor  $R_1$ ,  $I_1 = 0.5 \text{ A}$

The current through resistor  $R_2$ ,  $I_2 = 0.23 \text{ A}$

The current through resistor  $R_3$ ,  $I_3 = 0.7 \text{ A}$ .

For Fig-2

The current through resistor  $R_1$ ,  $I'_1 = 0.7 \text{ A}$ .

The current through resistor  $R_2$ ,  $I'_2 = 0.23 \text{ A}$

The current through resistor  $R_3$ ,  $I'_3 = 0.5 \text{ A}$ .

For fig-3

The current through resistor  $R_1$ ,  $I''_1 = 0.24 \text{ A}$

The current through resistor  $R_2$ ,  $I''_2 = 0.45 \text{ A}$

The current through resistor  $R_3$ ,  $I''_3 = 0.24 \text{ A}$

## Conclusion:

In this experiment we could see that the superposition theorem which states that "In a bilateral network with 2 or more than 2 energy sources, the circuit flowing at any point is the algebraic sum of all currents which would flow at that point if each source was considered separately and all other sources replaced at the time by impediment equal to their internal impedance." holds true and verified successfully. And we also saw some of the Limitations of superposition theorem.